

Digital Design

FSM Optimization

A. Sahu

Dept of Comp. Sc. & Engg.

Indian Institute of Technology Guwahati

<http://jatinga.iitg.ac.in/~asahu/cs221/>

Outline

- FSM Optimization: **State Minimization**
 - Row Matching method
 - **Partitioning method**
 - **Implication Chart**
- FSM Optimization : State Encoding
 - **Binary/Sequential, Gray, One-hot**
 - **Heuristic Based**


Partitioning Methods

State Minimization: Partitioning

- Form an initial partition (P_1) : that includes **all the** states.
- Form a 2nd partition (P_2)
 - By separating the states into two blocks based upon their output values.
- Form a third partition (P_3)
 - by separating the states into blocks corresponding to the next state values.
- Continue partitioning until
 - Two successive partitions are the same (i.e. $P_{N-1} = P_N$).
- All states in any one block are equivalent
 - Equivalent states can be combined into a single state.

State Minimization: Previous Example

 - Sequence Detector for 010 or 110
- After is asserted after each 3 bit input sequence if it consist of 110 or 010



State Minimization Example

Input	PS	NS		OUTPUT	
		X=0	X=1	X=0	X=1
Reset	S0	S1	S2	0	0
0	S1	S3	S4	0	0
1	S2	S5	S6	0	0
00	S3	S0	S0	0	0
01	S4	S0	S0	1	0
10	S5	S0	S0	0	0
11	S6	S0	S0	1	0

(S0 S1 S2 S3 S4 S5 S6)

State Minimization Example

Input	PS	NS		OUTPUT	
		X=0	X=1	X=0	X=1
Reset	S0	S1	S2	0	0
0	S1	S3	S4	0	0
1	S2	S5	S6	0	0
00	S3	S0	S0	0	0
01	S4	S0	S0	1	0
10	S5	S0	S0	0	0
11	S6	S0	S0	1	0

(S0 S1 S2 S3 S4 S5 S6)

(S0 S1 S2 S3 S5) (S4 S6)

State Minimization Example

Input	PS	NS		OUTPUT	
		X=0	X=1	X=0	X=1
Reset	S0	S1	S2	0	0
0	S1	S3	S4	0	0
1	S2	S5	S6	0	0
00	S3	S0	S0	0	0
01	S4	S0	S0	1	0
10	S5	S0	S0	0	0
11	S6	S0	S0	1	0

(S0 S1 S2 S3 S5)

0

1

(S1 S3 S5 S0 S0)

(S2 S4 S6

S0 S0)

(S0 S1 S2 S3 S4 S5 S6)

(S0 S1 S2 S3 S5)



(S4 S6)

(S1 S2)

(S0 S3 S5)


State Minimization Example

Input	PS	NS		OUTPUT	
		X=0	X=1	X=0	X=1
Reset	S0	S1	S2	0	0
0	S1	S3	S4	0	0
1	S2	S5	S6	0	0
00	S3	S0	S0	0	0
01	S4	S0	S0	1	0
10	S5	S0	S0	0	0
11	S6	S0	S0	1	0

  

State Minimization Example

Input	PS	NS		OUTPUT	
		X=0	X=1	X=0	X=1
Reset	S0	S1	S2	0	0
0	S1	S3	S4	0	0
1	S2	S5	S6	0	0
00	S3	S0	S0	0	0
01	S4	S0	S0	1	0
10	S5	S0	S0	0	0
11	S6	S0	S0	1	0

 

State Minimization Example

Input	PS	NS		OUTPUT	
		X=0	X=1	X=0	X=1
Reset	S0	S1	S2	0	0
0	S1	S3	S4	0	0
1	S2	S5	S6	0	0
00	S3	S0	S0	0	0
01	S4	S0	S0	1	0
10	S5	S0	S0	0	0
11	S6	S0	S0	1	0

(S0 S1 S2 S3 S4 S5 S6)

(S0)

(S4 S6)

0

1

(S0)

(S0)

(S1 S2)

0

1

(S3 S5)

(S4 S6)

(S3 S5)

0

1

(S0)

(S0)

State Minimization Example

Input	PS	NS		OUTPUT	
		X=0	X=1	X=0	X=1
Reset	S0	S1	S2	0	0
0	S1	S3	S4	0	0
1	S2	S5	S6	0	0
00	S3	S0	S0	0	0
01	S4	S0	S0	1	0
10	S5	S0	S0	0	0
11	S6	S0	S0	1	0

No further
partitions possible

(S0 S1 S2 S3 S4 S5 S6)

(S0)

(S4 S6)

0

1

(S0)

(S0)

(S1 S2)

0

1

(S3 S5)

(S4 S6)

(S3 S5)

0

1

(S0)

(S0)

State Minimization Example

Input	PS	NS		OUTPUT	
		X=0	X=1	X=0	X=1
Reset	S0	S1	S2	0	0
0	S1	S3	S4	0	0
1	S2	S5	S6	0	0
00	S3	S0	S0	0	0
01	S4	S0	S0	1	0
10	S5	S0	S0	0	0
11	S6	S0	S0	1	0

(S0 S1 S2 S3 S4 S5 S6)



(S0) (S1 S2) (S3 S5) (S4 S6)



(S0) (S1') (S3') (S4')

State Minimization Example


Input	PS	NS		OUTPUT	
		X=0	X=1	X=0	X=1
Reset	S0	S1'	S1'	0	0
0	S1'	S3	S4'	0	0
1	S2	S5	S4'	0	0
00	S3	S0	S0	0	0
01	S4'	S0	S0	1	0
10	S5	S0	S0	0	0
11	S4'	S0	S0	1	0

(S0) (S1 S2) (S3 S5) (S4 S6)





(S0) (S1') (S3') (S4')

Minimized FSM

 

Row Matching Method : Fallacies

  - Odd Parity Checker:
 - Two alternative state diagrams
 - Identical output behavior on all input strings
 - FSMs are *equivalent*, but require different implementations



**Design state diagram
without concern for
of states, Reduce
later**

Partitioning Method

Present State	Next State		Output
	X=0	X=1	
s_0	s_0	s_1	0
s_1	s_1	s_2	1
s_2	s_2	s_1	0


($s_0s_1s_2$)
Based on output
(s_0s_2) (s_1)

Partitioning Method

Present State	Next State		Output
	X=0	X=1	
s_0	s_0	s_1	0
s_1	s_1	s_2	1
s_2	s_2	s_1	0

($s_0 s_1 s_2$)
Based on output
($s_0 s_2$) (s_1)

 Was not possible with Row matching method



s_0, s_2 are same

$\{s_0 s_2\}, \{s_1\} \Rightarrow \{s_0'\}, \{s_1\}$

But possible with Partitioning method


Some Definitions

- **State Equivalence:** S1 and S2 are equivalent if for every input sequence applied to machine goes to same NS and Output
 - If $S1(t+1)=S2(t+1)$ and $Z1=Z2$ then $S1=S2$
- **Distinguishable States:** Two states S1 and S2 are Distinguishable *if and only if* there exist at least one finite input sequence which produce different outputs from S1 and S2

Implication Chart Methods

Sequence Detector Example

 - Sequence Detector for 010 or 110
- After is asserted after each 3 bit input sequence if it consist of 110 or 010





FSM :Tabular Form

Input	PS	NS		OUTPUT	
		X=0	X=1	X=0	X=1
Reset	S0	S1	S2	0	0
0	S1	S3	S4	0	0
1	S2	S5	S6	0	0
00	S3	S0	S0	0	0
01	S4	S0	S0	1	0
10	S5	S0	S0	0	0
11	S6	S0	S0	1	0

Implication Chart Method

Enumerate all possible combinations of states taken two at a time

Next States
Under all
Input
Combinations

  

Naive Data Structure: X_{ij} will be the same as X_{ji}
Also, can eliminate the diagonal


Implication Chart Method

Filling in the Implication Chart

- Entry X_{ij} — Row is S_i , Column is S_j
- S_i is equivalent to S_j if outputs are the same and next states are equivalent
- X_{ij} contains the next states of S_i, S_j which must be equivalent if S_i and S_j are equivalent
- If S_i, S_j have different output behavior, then X_{ij} is crossed out

Implication Chart Method

 If S_i, S_j have different output behavior, then X_{ij} is crossed out




Starting Implication Chart

Input	PS	NS		OUTPUT	
		X=0	X=1	X=0	X=1
Reset	S0	S1	S2	0	0
0	S1	S3	S4	0	0
1	S2	S5	S6	0	0
00	S3	S0	S0	0	0
01	S4	S0	S0	1	0
10	S5	S0	S0	0	0
11	S6	S0	S0	1	0

Implication Chart Method

If S_i, S_j have different output behavior, then X_{ij} is crossed out

 
- S4 have different output behavior with S0, S1, S2, S3, S5
- S6 have different output behavior with S0, S1, S2, S3, S5



Starting Implication Chart

Input	PS	NS		OUTPUT	
		X=0	X=1	X=0	X=1
Reset	S0	S1	S2	0	0
0	S1	S3	S4	0	0
1	S2	S5	S6	0	0
00	S3	S0	S0	0	0
01	S4	S0	S0	1	0
10	S5	S0	S0	0	0
11	S6	S0	S0	1	0

Implication Chart Method

 

Starting Implication Chart


Fill other X_{ij} Based on Next State Transaction

S0 : S1, S2 when X=0, 1

S1 : S3, S4 when X=0, 1

Input	PS	NS		OUTPUT	
		X=0	X=1	X=0	X=1
Reset	S0	S1	S2	0	0
0	S1	S3	S4	0	0
1	S2	S5	S6	0	0
00	S3	S0	S0	0	0
01	S4	S0	S0	1	0
10	S5	S0	S0	0	0
11	S6	S0	S0	1	0

Implication Chart Method

 


Starting Implication Chart

Fill others X_{ij} Based on Next State Transaction

Input	PS	NS		OUTPUT	
		X=0	X=1	X=0	X=1
Reset	S0	S1	S2	0	0
0	S1	S3	S4	0	0
1	S2	S5	S6	0	0
00	S3	S0	S0	0	0
01	S4	S0	S0	1	0
10	S5	S0	S0	0	0
11	S6	S0	S0	1	0

Implication Chart Method

 


**S2 and S4
have
different
I/O
behavior**

**This implies that
S1 and S0 cannot
be combined**

Marked with Cross

Implication Chart Method

 


**S2 and S4
have
different
I/O
behavior**


**This implies that
S1 and S0 cannot
be combined**

Marked with Cross

Implication Chart Method

 

Implication Chart Method

 


**S2 and S6
have different
I/O behavior**


**This implies that
S2 and S0 cannot
be combined**

Marked with Cross

Implication Chart Method

 


Implication Chart Method

 

S1 S0 is already crossed

So S3 S0


Implication Chart Method

 

S4 S0 is already crossed

So S3 S1


Implication Chart Method

 

S6 S0 is already crossed

So S3 S2


Implication Chart Method

 

S2 S0 is already crossed


So S5 S0

Implication Chart Method

 


Second Pass Adds No New Information

Implication Chart Method

 

Second Pass Adds No New Information

Implication Chart Method

 


S3 and S5 are equivalent
S4 and S6 are equivalent
S1 and S2 are equivalent

Second Pass Adds No New Information


Final : Reduce State Table

Input	PS	NS		OUTPUT	
		X=0	X=1	X=0	X=1
Reset	S0	S1	S2	0	0
0	S1	S3	S4	0	0
1	S2	S5	S6	0	0
00	S3	S0	S0	0	0
01	S4	S0	S0	1	0
10	S5	S0	S0	0	0
11	S6	S0	S0	1	0

 

Input	PS	NS		Output	
		X=0	X=1	X=0	X=1
Reset	S0	S1'	S1'	0	0
0 or 1	S1'	S3'	S4'	0	0
00 or 10	S3'	S0	S0	0	0
01 or 11	S4'	S0	S0	1	0

Minimized FSM

 

Outline

- FSM Optimization: State Minimization
 - Row Matching method
 - Partitioning method
 - Implication Chart
- **FSM Optimization : State Encoding**
 - Binary/Sequential, Gray, One-hot
 - Heuristic Based


State Encoding/Assignment

State assignment

- State encoding:
 - Assigning unique binary value to each state
 - So that we can implement FSM
- Since we don't care about the actual flip-flop values for each state
- We can assign each state to any binary number we like **as long as**
 - Each state is assigned a unique binary number

 Example of FSM: 3 cycle Laser

- Require 4 States
- Assigning unique binary value/code to each state
- Options available : 4!



State Encoding Example

- Four states
S0, S1, S2, S3
- 4! options

SL	S0	S1	S2	S3
1	00	01	10	11
2	00	01	11	10
3	00	10	01	11
4	00	10	11	01
5	00	11	01	10
6	00	11	10	01
7	01	00	11	10
8	01	00	10	11
9	01	10	11	00
10	01	10	00	11
11	01	11	10	00
12	01	11	00	11

SL	S0	S1	S2	S3
13	10	01	00	11
14	10	01	11	00
15	10	00	01	11
16	10	00	11	01
17	10	11	01	00
18	10	11	00	01
19	11	00	01	10
20	11	00	10	01
21	11	10	01	00
22	11	10	00	01
23	11	01	10	00
24	11	01	00	11

State assignment

- Since we don't care about the actual flip-flop values for each state we can assign each state to any binary number we like **as long as** each state is assigned a unique binary number
- Suppose a FSM have 6 states: Modulo 6 Counter
- If we use 3 bits to encode the 6 states, we have

$$\binom{8}{6} = \frac{8!}{6!(8-6)!}$$

possible choosing the 6 states from 8 total state

- Than encodings

State Encoding

- The cost & delay of FSM implementation depends on encoding of symbolic states.
 - e.g., 4 states can be encoded in $4! = 24$ different ways
- There are more than $n!$ different encodings for n states.
 - **Exploration of all encodings is impossible**, therefore heuristics are used
- Heuristics Used
 - One-hot encoding, Minimum-bit change, Prioritized adjacency

State assignment

state	Encoding 1 (binary)	Encoding 2 (Gray)	Encoding 3
a	000	000	000
b	001	001	100
c	010	011	010
d	011	010	101
e	100	110	011

State Encoding

- Binary and Gray encoding use the minimum number of bits for state register
- Gray and Johnson code: Two adjacent codes differ by only one bit
 - Reduce simultaneous switching
 - Reduce crosstalk, Reduce glitch

One-hot encoding

- One flip-flop per state encoding
- Leads to greater number of flip-flops than binary encoding but possibly to simpler logic

State Assignment Problem

- Some state assignments are better than others.
- The state assignment influences the complexity of the state machine.
 - The combinational logic required in the state machine design is dependent on the state assignment.
- Types of state assignment
 - Binary encoding: 2^N states $\rightarrow$ N Flip-Flops
 - Gray-code encoding: 2^N states $\rightarrow$ N Flip-Flops
 - One-hot encoding: N states $\rightarrow$ N Flip-Flops

FSM: State Assignment

Example

Design a FSM that detects a sequence of two or more consecutive ones on an input bit stream.


The FSM should output a 1 when the sequence is detected, and a 0 otherwise.

FSM: State Assignment

Input: 0 1 1 1 0 1 0 1 1 0 1 1 1 0 1 ...

Output: 0 0 1 1 0 0 0 0 1 0 0 1 1 0 0 ...

FSM: State Assignment

 

State Diagram

FSM: State Assignment

Present State	Next State		Output
	w = 0	w = 1	
s_0	s_0	s_1	0
s_1	s_0	s_2	0
s_2	s_0	s_2	1

State Table

FSM: State Assignment #1

State Assigned Table

Present State			Next State						Output
			w = 0			w = 1			
	Q_A	Q_B		Q_A^+	Q_B^+		Q_A^+	Q_B^+	z
S_0	0	0	S_0	0	0	S_1	0	1	0
S_1	0	1	S_0	0	0	S_2	1	0	0
S_2	1	0	S_0	0	0	S_2	1	0	1
	1	1		d	d		d	d	d

Using Binary Encoding
for the State Assignment

$$\begin{aligned}D_B &= wQ'_A Q'_B \\D_A &= w(Q_A + Q_B) \\z &= 0\end{aligned}$$

FSM: State Assignment #2

State Assigned Table

Present State			Next State						Output
			w = 0			w = 1			
	Q_A	Q_B		Q_A^+	Q_B^+		Q_A^+	Q_B^+	z
S_0	0	0	S_0	0	0	S_1	0	1	0
S_1	0	1	S_0	0	0	S_2	1	1	0
S_2	1	1	S_0	0	0	S_2	1	1	1
	1	0		d	d		d	d	d

$$D_A = w \cdot Q_B$$

$$D_B = w$$

$$Z = Q_A$$

Using Gray-code Encoding
for the State Assignment

FSM: State Assignment #3

State Assigned Table

Present State				Next State							
				w = 0				w = 1			
	Q_A	Q_B	Q_C		Q_A^+	Q_B^+	Q_C^+		Q_A^+	Q_B^+	Q_C^+
S_0	0	0	1	S_0	0	0	1	S_1	0	1	0
S_1	0	1	0	S_0	0	0	1	S_2	1	0	0
S_2	1	0	0	S_0	0	0	1	S_2	1	0	0

Using One-hot Encoding
for the State Assignment

For each state only one flip-flop is set to 1.

The remaining combination of state

$$D_A = w \cdot Q_C'$$


$$D_B = w \cdot Q_C$$

$$D_C = w'$$

State Encoding

#	Binary	Gray	Johnson	One-hot
0	000	000	0000	00000001
1	001	001	0001	00000010
2	010	011	0011	00000100
3	011	010	0111	00001000
4	100	110	1111	00010000
5	101	111	1110	00100000
6	110	101	1100	01000000
7	111	100	1000	10000000

Johnson Counter

 

Thanks