

# Digital Design

## RTL Design: Sequential Multiplier

A. Sahu

Dept of Comp. Sc. & Engg.

Indian Institute of Technology Guwahati

<http://jatinga.iitg.ac.in/~asahu/cs221/>

# Outline

- Classic Example : Sequential Multiplier
- Verilog Code for Multiplier
- FPGA: Introduction

RTL/ASM Classic example :  
8 bit Sequential Multiplier  
With Verilog Code

Ref: Mano Book

# RTL: Multiplier Example

- Example: (101 x 011)
- Partial product sum for  $n$  digits
  - requires adding up to  $n$  digits (with carries) in a column.
- $n \times m$  digit multiply generates
  - up to an  $m + n$  digit result

- Partial products are:  
**101 x 0, 101 x 1, and 101 x 1**

|          |          |          |          |          |          |          |  |
|----------|----------|----------|----------|----------|----------|----------|--|
|          |          |          |          | <b>1</b> | <b>0</b> | <b>1</b> |  |
|          |          |          | <b>x</b> | <b>0</b> | <b>1</b> | <b>1</b> |  |
|          |          |          |          |          |          |          |  |
|          |          |          |          | <b>1</b> | <b>0</b> | <b>1</b> |  |
|          |          |          | <b>1</b> | <b>0</b> | <b>1</b> |          |  |
|          | <b>0</b> | <b>0</b> | <b>0</b> |          |          |          |  |
|          |          |          |          |          |          |          |  |
| <b>0</b> | <b>0</b> | <b>1</b> | <b>1</b> | <b>1</b> | <b>1</b> |          |  |

# Example (1 0 1) x (0 1 1) Again

- Reorganizing example to follow hardware algorithm:

|   |   |   |   |   |   |   |   |  |                                        |  |
|---|---|---|---|---|---|---|---|--|----------------------------------------|--|
|   | x | 1 | 0 | 1 |   |   |   |  |                                        |  |
|   |   | 0 | 1 | 1 |   |   |   |  |                                        |  |
| → | 0 | 0 | 0 | 0 |   |   |   |  | Clear C    A                           |  |
| → | + | 1 | 0 | 1 |   |   |   |  | Multiplier0 = 1 => Add B               |  |
| → | 0 | 1 | 0 | 1 |   |   |   |  | Addition                               |  |
| → | 0 | 0 | 1 | 0 | 1 |   |   |  | Shift Right (Zero-fill C)              |  |
| → | + | 1 | 0 | 1 |   |   |   |  | Multiplier1 = 1 => Add B               |  |
| → | 0 | 1 | 1 | 1 | 1 |   |   |  | Addition                               |  |
| → | 0 | 0 | 1 | 1 | 1 | 1 |   |  | Shift Right                            |  |
| → | 0 | 0 | 0 | 1 | 1 | 1 | 1 |  | Multiplier2 = 0 => No Add, Shift Right |  |

# Binary Multiplication

- Polynomial Multiplication
  - You can think Binary number A, B as polynomials
  - $A(X) = A_{n-1} \cdot 2^{n-1} + \dots + A_2 \cdot 2^2 + A_1 \cdot 2^1 + A_0 \cdot 2^0$
  - Multiply polynomial to get another one
  - Time complexity:  $O(n^2)$  Basic serial Algorithm,  $O(n^{1.5})$  for divide conquer approach,  $O(n \lg n)$  using FFT
- Booth Algorithm reduce number Partial addition
  - 99 Represent using 100-1, 95 is 100-5
  - 111 represent as 1000-1 in binary: possibly reduce number addition/sub

# Booth's Encoding

- Recall grade school trick
  - When multiplying by 9:
    - Multiply by 10 (easy, just shift digits left), Subtract once
  - E.g.  $123454 \times 9 = 123454 \times (10 - 1) = 1234540 - 123454$
- Booth's algorithm applies same principle
  - in binary, just '1' and '0'

# Booth's Encoding

- Search for a run of '1' bits in the multiplier
  - E.g. '01110' has a run of 3 '1' bits in the middle
  - Multiplying by '01110' (14 in decimal) is equivalent to multiplying by 8 and subtracting twice, since  $14 \times m = (16 - 2) \times m = 16m - 2m$
  - Convert to two shifts and one subtraction
- Hence, iterate right to left and:
  - Subtract multiplicand from product at first '1'
  - Add multiplicand to product after last '1'
  - Don't do either for '1' bits in the middle



# Booth's Algorithm

| Current bit | Bit to right | Explanation            | Example              | Operation      |
|-------------|--------------|------------------------|----------------------|----------------|
| 1           | 0            | Begins run of '1'      | 0000111 <b>1</b> 000 | Subtract       |
| 1           | 1            | Middle of run of '1'   | 000011 <b>11</b> 000 | <b>Nothing</b> |
| 0           | 1            | End of a run of '1'    | 000 <b>0</b> 1111000 | Add            |
| 0           | 0            | Middle of a run of '0' | 0 <b>00</b> 01111000 | <b>Nothing</b> |

# Booth's Encoding Example

0110111111101111111010111100

a x s a x x x x x x s a x x x x x x s a s a x x x s x x


x a a x a a a a a a x a a a a a a x a x a a a a x x

**Booth Encoding**  
**10 ADD/SUB**

**Less work:  
Power  
Saving**

**Normal Sequential Multiplier**  
**21 ADD**

 
# Sequential Multiplier: High Level Algorithm



## Control Algorithm:

1.  $P \leftarrow 0$ ,  $A \leftarrow$  multiplicand,  $B \leftarrow$  multiplier **//Initialization**
2. **If** (LSB of  $B == 1$ ) add  $A$  to  $P$   
**else** add 0
3. Shift  $[P][B]$  right 1
4. Repeat steps 2 and 3 for  $n-1$  times.
5.  $[P][B]$  has product.

# Multiplier Example: Block Diagram

 


## Multiplier Example: Operation

- Step1: The multiplicand (top operand) is loaded into register B.
- Step2: The multiplier (bottom operand) is loaded into register Q.
- Step3: Register C || A is initialized to 0 when G becomes 1.
- Step4: The partial products are summed iteratively in register C || A || Q.

## Multiplier Example: Operation

- Step5: Each multiplier bit, beginning with the LSB, is processed (if bit is 1, use adder to add B to partial product; if bit is 0, do nothing)
- Step6: C || A || Q is shifted right using the shift register
  - Partial product bits fill vacant locations in Q as multiplier is shifted out
  - If overflow during addition, the outgoing carry is recovered from C during the right shift
- Step 7: Steps 5 and 6 are repeated until Ctr P = 0
  - Counter P is initialized in step 4 to  $n - 1$ ,  $n$  = number of bits in multiplier

# Multiplier Example: ASM Chart

 

# Multiplier Example: ASM Chart (continued)

- Combined Mealy - Moore output model
- **IDLE - state**
  - Input G is used as the condition for starting the multiplication, and
  - *C, A, and P are initialized and Load B, Load Q*
- **MUL0 - state**
  - Conditional addition is performed based on the value of  $Q_0$ .
- **MUL1 - state**
  - Right shift is performed to capture the partial product and position the next bit of the multiplier in  $Q_0$
  - the terminal count of 0 for down counter P is used to sense completion or continuation of the multiply.



# Multiplier Example: Control Signal Table

| Module | Micro Operations                                                                     | Control Signal Name                | Control Expression                    |
|--------|--------------------------------------------------------------------------------------|------------------------------------|---------------------------------------|
| Reg A  | $A \leftarrow 0$<br>$A \leftarrow A + B$<br>$C    A    Q \leftarrow sr(C    A    Q)$ | Load_regs<br>Add_regs<br>Shift CAQ | IDLE.G<br>MUL0.Q <sub>0</sub><br>MUL1 |
| Reg B  | $B \leftarrow IN$                                                                    | Load_regs                          | LOAD_B                                |
| FF C   | $C \leftarrow 0$<br>$C \leftarrow Cout$                                              | Clear C<br>Load                    | IDLE.G+MUL1<br>--                     |
| Reg Q  | $Q \leftarrow IN$<br>$C    A    Q \leftarrow sr(C    A    Q)$                        | Load_regs<br>ShiftCAQ              | LOAD_Q                                |
| Ctr P  | $P \leftarrow N-1$<br>$P \leftarrow P-1$                                             | Load_regs<br>Decr_P                | MUL1                                  |

# Multiplier Example: Control Circuit

| PS   | PS | Inputs |    |   | NS | Ready | Load<br>Regs | Decr_P | Add_regs | Shift_C<br>AQ |
|------|----|--------|----|---|----|-------|--------------|--------|----------|---------------|
|      |    | G      | Q0 | Z |    |       |              |        |          |               |
| Idle | 00 | 0      | x  | X | 00 | 1     |              |        |          |               |
| Idle | 00 | 1      | X  | x | 01 | 1     | 1            |        |          |               |
| Mul0 | 01 | x      | 0  | X | 10 |       |              | 1      |          |               |
| Mul0 | 01 | x      | 1  | X | 10 |       |              |        | 1        |               |
| Mul1 | 10 | x      | x  | 0 | 01 |       |              | 1      |          | 1             |
| Mul1 | 10 | x      | x  | 1 | 00 |       |              | 1      |          | 1             |

Ready=Idle


Load\_Regs=Idle.G

Decr\_P=Mul0

Add\_regs=Mul0.Q<sub>0</sub>

ShiftCAQ=Mul1

# Multiplier Example: Control Circuit

 

$$N1 = D_1' D_0$$

$$N0 = D_1' D_0' G + D_1 D_0' Z'$$

$$\text{Ready} = \text{Idle}$$

$$\text{Load\_Regs} = \text{Idle} \cdot G$$

$$\text{Decr\_P} = \text{Mul1}$$

$$\text{Add\_regs} = \text{Mul0} \cdot Q_0$$

$$\text{ShiftCAQ} = \text{Mul1}$$

# Verilog Code For Multiplier

//IO Description

```
module Seq_Bin_Mult(Product, Ready, Multiplicand, Multiplier,  
Start, clock, reset_b);
```

```
    parameter dp_width = 5; // Set to width of datapath
```

```
    parameter BC_size = 3; // Size of bit counter
```

```
    output [2*dp_width -1: 0] Product;
```

```
    output Ready;
```

```
    input [dp_width -1: 0] Multiplicand, Multiplier;
```

```
    input Start, clock, reset_b;
```

# Verilog Code For Multiplier

```
//ASM State One Hot Encoding
```

```
parameter S_idle=3'b001, S_add= 3'b010, S_shift=3'b100;
```

```
reg [2: 0] state, next_state;
```

```
//Data Path Components
```

```
reg [dp_width -1: 0] A, B, Q; // Sized for datapath
```

```
reg C;
```

```
reg [BC_size -1: 0] P;
```

```
reg Load_regs, Decr_P, Add_regs, Shift_regs;
```

```
// Miscellaneous combinational logic
```

```
assign Product = {A, Q};
```

```
wire Zero = (P == 0); // counter is zero
```

```
wire Ready = (state == S_idle); // controller status
```

# Verilog Code For Multiplier

```
always @ (posedge clock, negedge reset_b) // control unit
if (~reset_b) state <= S_idle; else state <= next_state;
always @ (state, Start, Q[0], Zero) begin
    next_state=S_idle;
    Load_regs=0; Decr_P=0; Add_regs=0;Shift_regs = 0;
    case (state)
        S_idle: begin if (Start) next_state=S_add; Load_regs=1; end
        S_add: begin next_state = S_shift; Decr_P = 1;
                if (Q[0]) Add_regs = 1; end
        S_shift: begin Shift_regs = 1; if (Zero) next_state = S_idle;
                  else next_state = S_add; end
        default : next_state = S_idle;
    endcase
end
```

# Verilog Code For Multiplier

```
// datapath unit
```

```
always @ (posedge clock) begin
```

```
    if (Load_regs) begin
```

```
        P <= dp_width; A <= 0; C <= 0;
```

```
        B <= Multiplicand; Q <= Multiplier;
```

```
    end
```

```
    if (Add_regs) {C, A} <= A + B;
```

```
    if (Shift_regs) {C, A, Q} <= {C, A, Q} >> 1;
```

```
    if (Decr_P) P <= P -1;
```

```
end
```

```
endmodule
```

# Verilog Code For Multiplier : Test1

*// Test bench for the binary multiplier*

```
module tb_Seq_Bin_Mult;
```

```
    parameter dp_width = 5; // Set to width of datapath
```

```
    wire [2*dp_width -1: 0] Product; // Output from multiplier
```

```
    wire Ready;
```

```
    reg [dp_width -1: 0] Multiplicand, Multiplier; // Inputs
```

```
    reg Start, clock, reset_b;
```

```
    // Instantiate multiplier
```

```
    Seq_Bin_Mult M0 (Product, Ready, Multiplicand, Multiplier,  
                    Start, clock, reset_b);
```

```
    // Generate stimulus waveforms
```

```
    initial #200 $finish ;
```



# Verilog Code For Multiplier: Test1

**Initial begin**

Start = 0;

reset\_b = 0; #2 Start = 1; reset\_b = 1;

Multiplicand= 5'b10111; Multiplier = 5'b10011; **//23\*19=437**

#10 Start = 0;

**end**

**Initial begin** clock = 0; repeat (26) #5 clock = ~clock; **end**

**always @ (posedge clock)** // Display results

**\$strobe** ("C=%b A=%b Q=%b P=%b time=%0d",

M0.C,M0.A,M0.Q,M0.P, **\$time**);

**endmodule**

# Verilog Code For Multiplier: Result 1

```
$ iverilog SeqMult.v
```

```
$/a.out
```

```
C=0 A=00000 Q=10011 P=101 time=5  
C=0 A=10111 Q=10011 P=100 time=15  
C=0 A=01011 Q=11001 P=100 time=25  
C=1 A=00010 Q=11001 P=011 time=35  
C=0 A=10001 Q=01100 P=011 time=45  
C=0 A=10001 Q=01100 P=010 time=55  
C=0 A=01000 Q=10110 P=010 time=65  
C=0 A=01000 Q=10110 P=001 time=75  
C=0 A=00100 Q=01011 P=001 time=85  
C=0 A=11011 Q=01011 P=000 time=95  
C=0 A=01101 Q=10101 P=000 time=105
```

//Multiplying 10111 (23)  
with 10011 (19) will result  
110110101 (437)

//result is  
CAQ= 0 **01101 10101**

# Vector Dot Product Unit: VDPU

- Vector Dot Product
- Common for Matrix Mul, Neural Network, CNN, DNN and Many machine Learning
- $S = \sum_{i=0}^{N-1} W_i X_i$
- Each cycle one Multiplication and Addition

# Verilog Code For VDPU

```
module VDPU (  
    input clk, input reset,  
    input [7:0] num1,  
    input [7:0] num2,  
    output reg [15:0] result  
);  
  
reg [15:0] temp_result; // result  
reg [2:0] count; // counter for multiplication
```

# Verilog Code For VDPU

```
always @(posedge clk or posedge reset) begin
    if (reset) begin
        result <= 16'd0;    temp_result <= 16'd0;    count <= 3'd0;
    end
    else begin    if (count < 3'd7) begin
        temp_result <= num1 * num2;
        result <= result + temp_result;
        count <= count + 1;
    end
end
end
endmodule
```

**Thanks**