
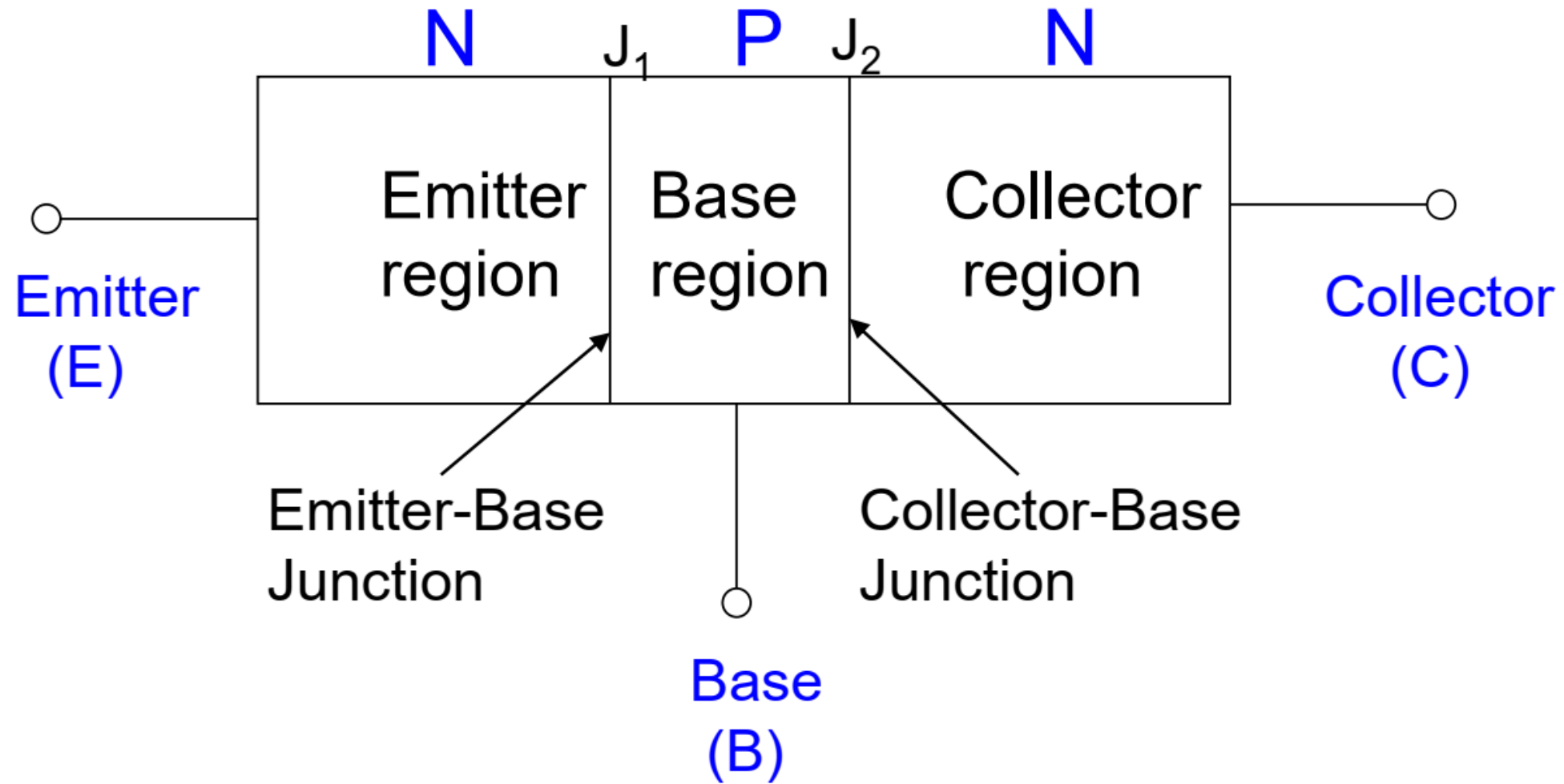


Bipolar Junction Transistor

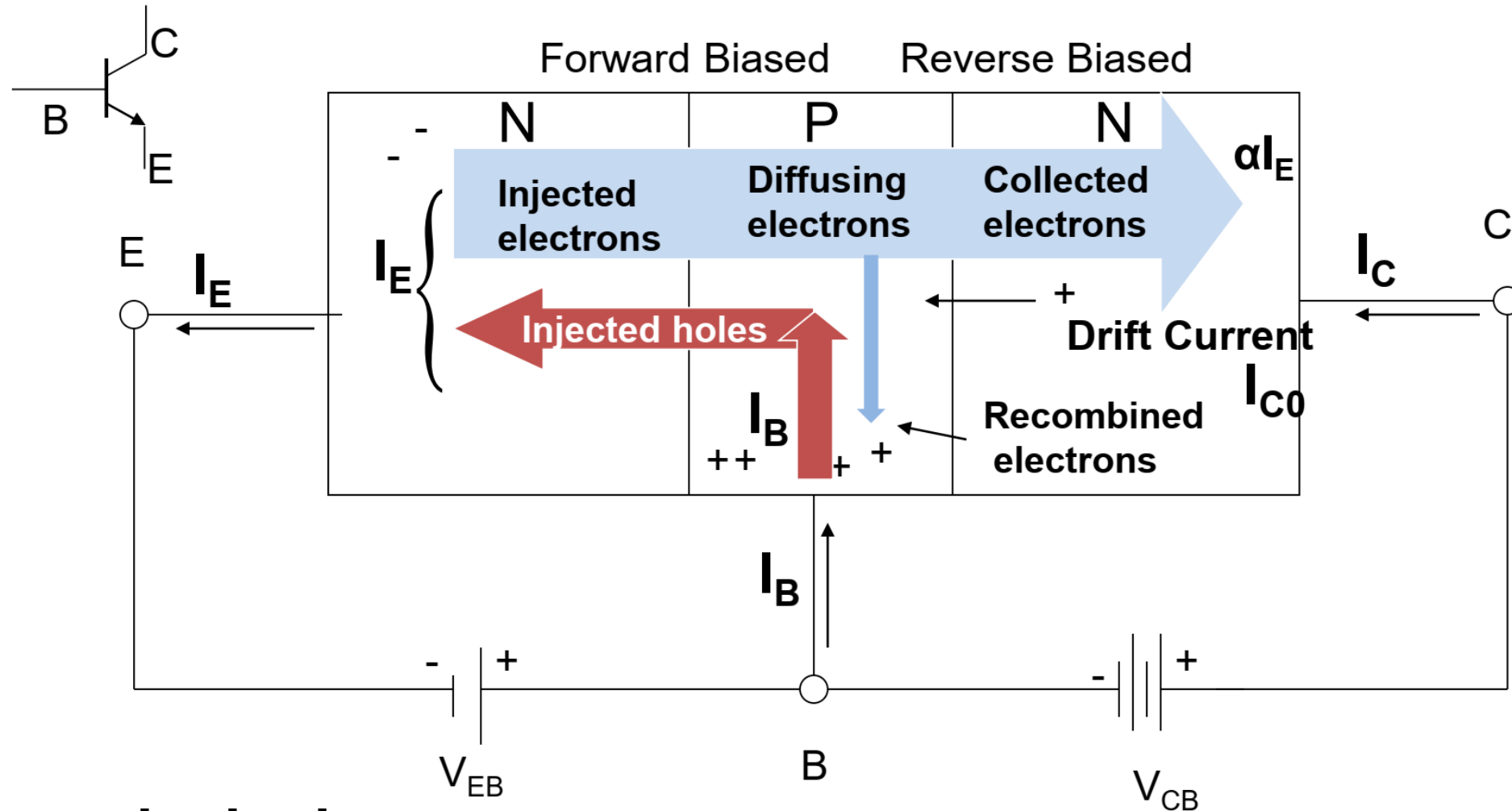


Operation of an NPN Transistor in the Active mode



$$I_E = I_B + I_C$$

$$I_C = \alpha I_E + I_{C0}$$

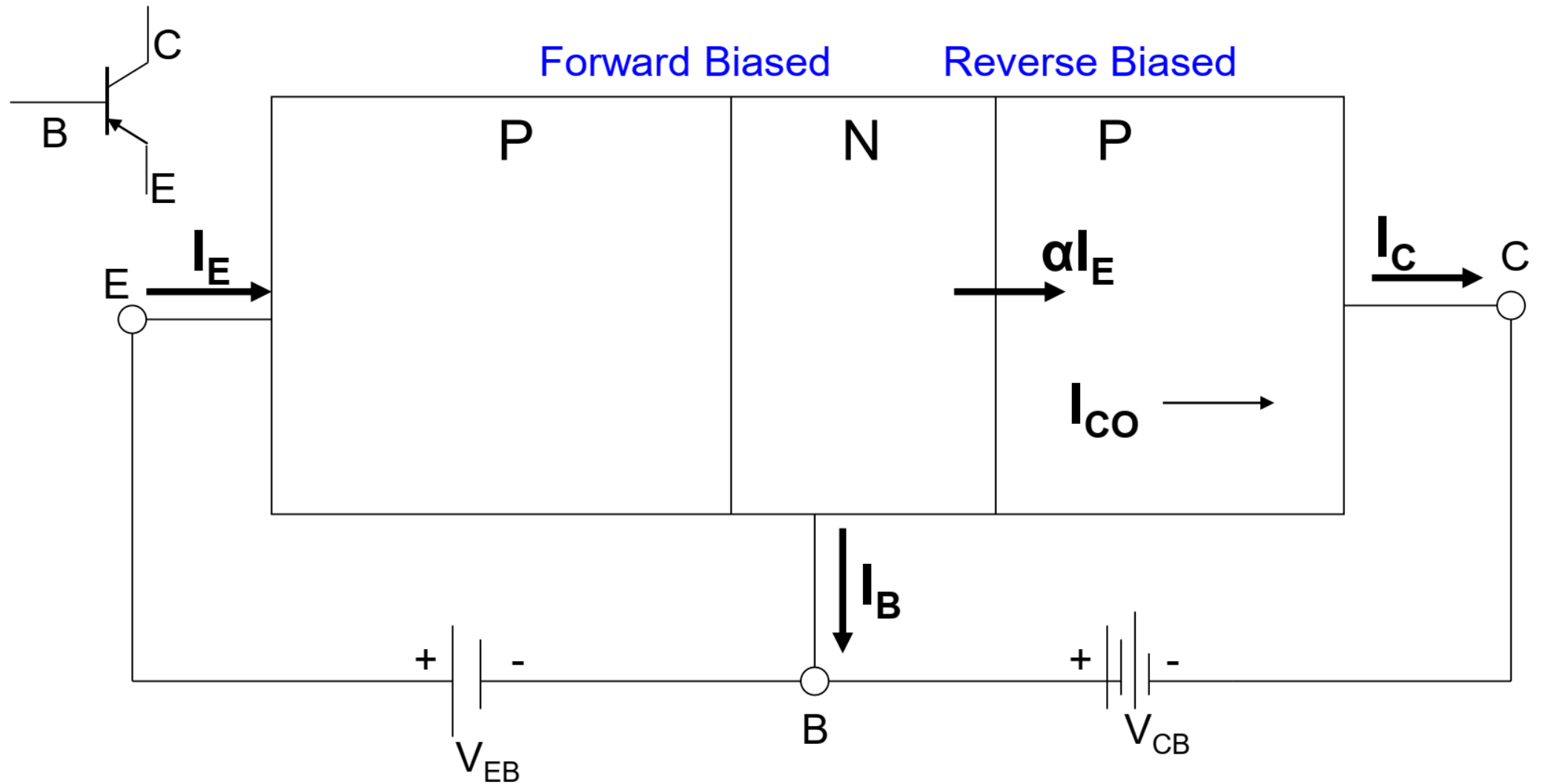

$$I_E = I_B + I_C$$

$$I_C = \alpha I_E + I_{CO}$$

α is the fraction of the total emitter current which goes from the emitter, across the base, to the collector

$$I_C = \alpha I_E + I_{CO}$$

$$I_E = I_B + I_C$$

$$I_C = \alpha(I_B + I_C) + I_{CO}$$

$$(1 - \alpha)I_C = \alpha I_B + I_{CO}$$

Transistor in Active Mode

$$I_C = \frac{\alpha}{1 - \alpha} I_B + \frac{1}{1 - \alpha} I_{CO}$$

Define $\beta = \frac{\alpha}{1 - \alpha}$

$$I_C = \beta I_B + (\beta + 1)I_{CO}$$

A Transistor may be operated in three different configurations :



Common Base (CB)

Common Emitter (CE)



Common Collector (CC)



Common Base (CB) Transistor Configuration

PNP

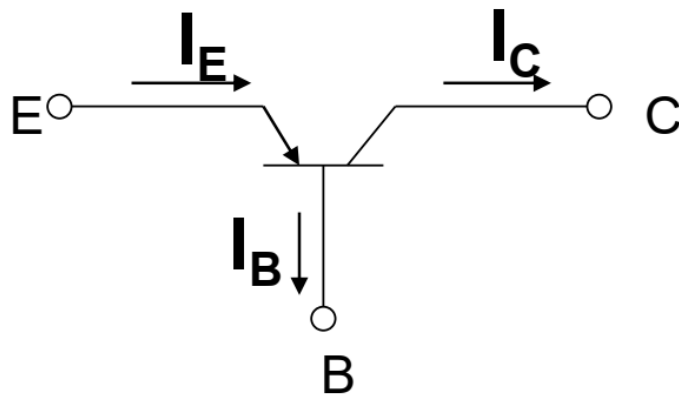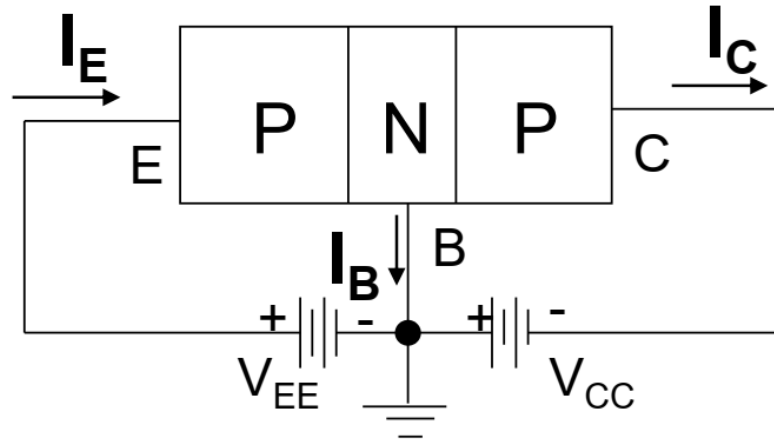

NPN

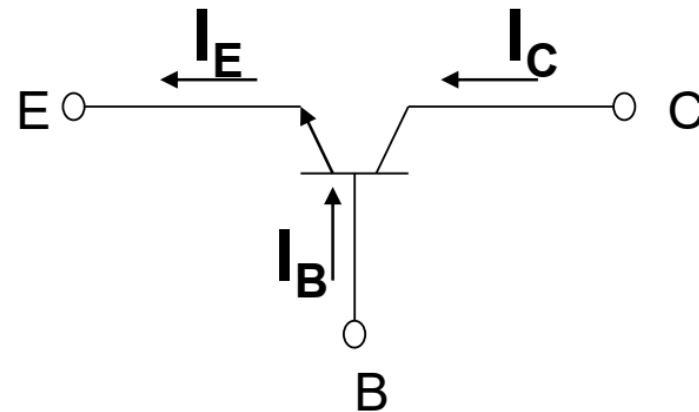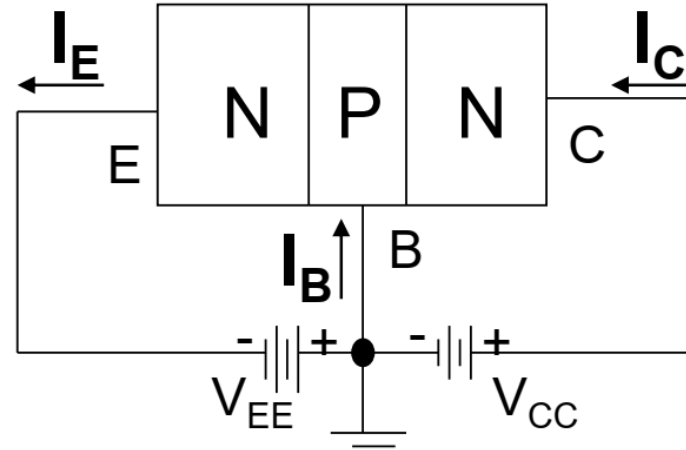

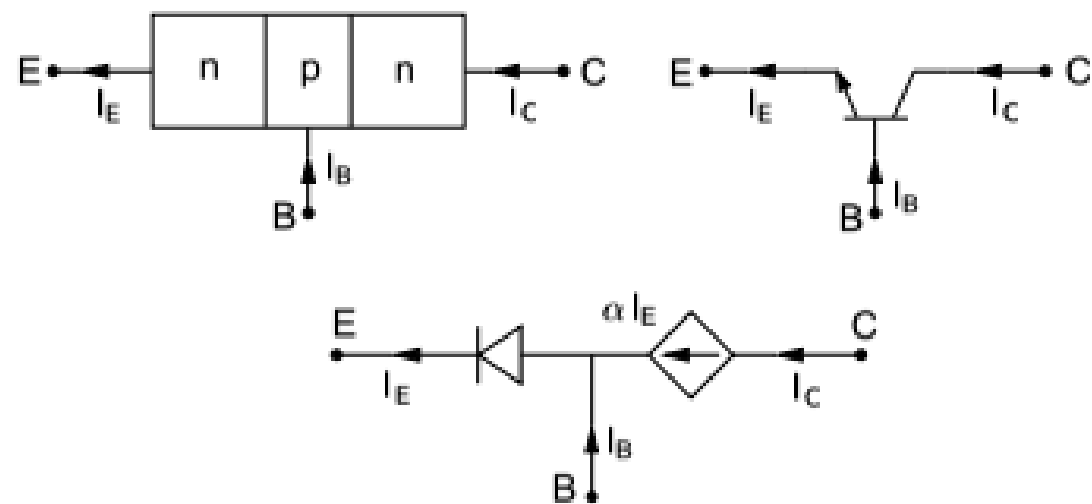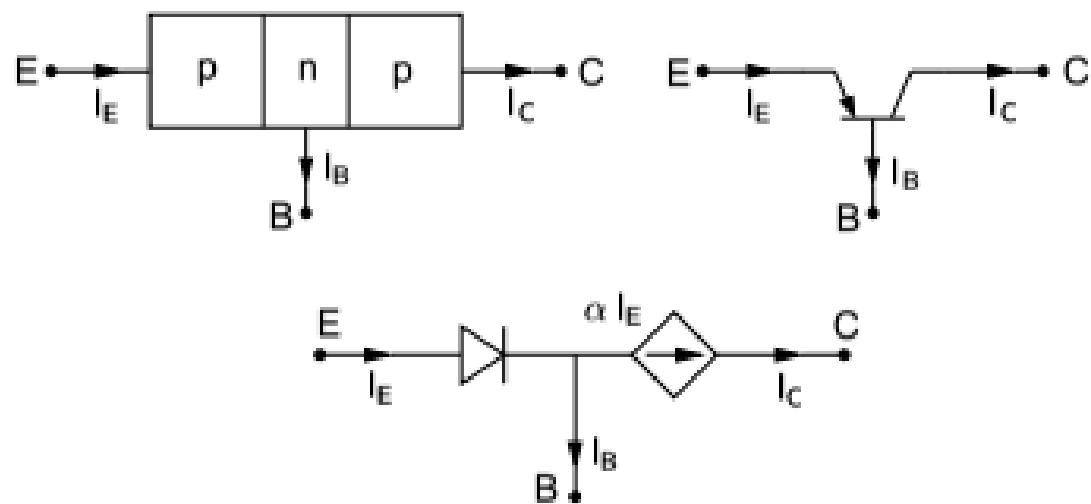

Common Emitter (CE) Transistor Configuration

