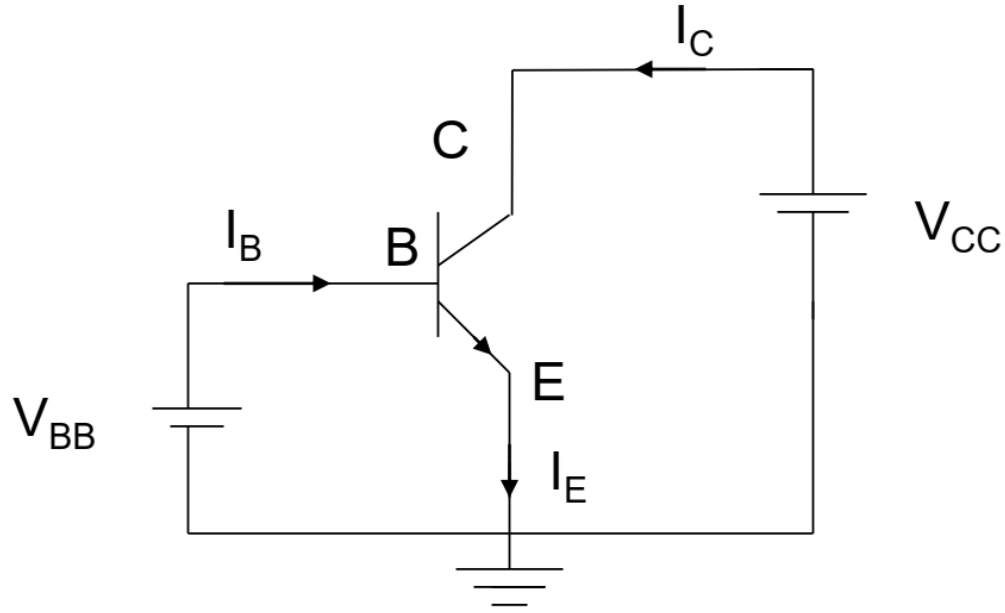


CE Transistor - npn



Common Emitter (CE) Transistor

β = Common emitter current
amplification factor
 $= I_C / I_B$

Current Gain of the Transistor

$$I_C = \beta I_B + (\beta + 1) I_{CO}$$

$$\beta = \alpha / (1 - \alpha)$$

Example -

For $\alpha = 0.98$,


$$\beta = 49$$

β increases rapidly as $\alpha \rightarrow 1$

Output characteristics of CE Amplifier

$I_C < \beta I_B$
Saturation region

Cutoff Region

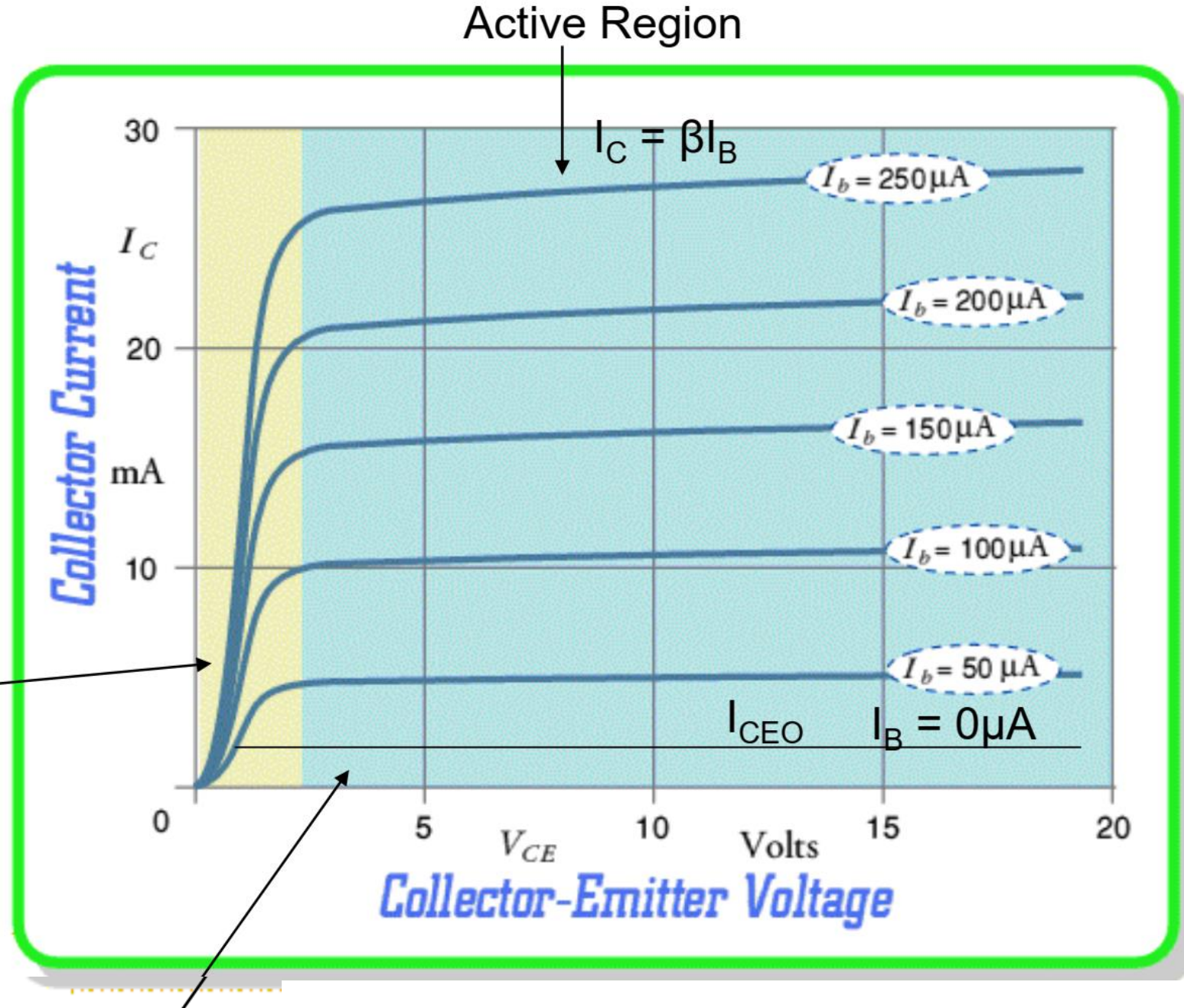

Transistor in Cutoff Region

Both the BC and the BE junctions are reverse biased

$$I_E = 0$$

$$I_C = I_{CO} \approx 0$$

$$I_B = -I_C = -I_{CO} \approx 0$$

Transistor in Saturation Region

*Both the BC and BE junctions are forward biased
and $I_C < \beta I_B$*

$$V_{BE} \approx 0.7 \text{ V}$$

$$V_{BC} \approx 0.6 \text{ V}$$

$$V_{CE} \approx 0.1$$



Transistor in Active Region


The BE junction is forward biased but the BC junction is reverse biased and $I_C \approx \beta I_B$

$$V_{BE} = 0.7 \text{ V}$$

Transistor is operated in this region when we want to use it as an amplifier!

Example

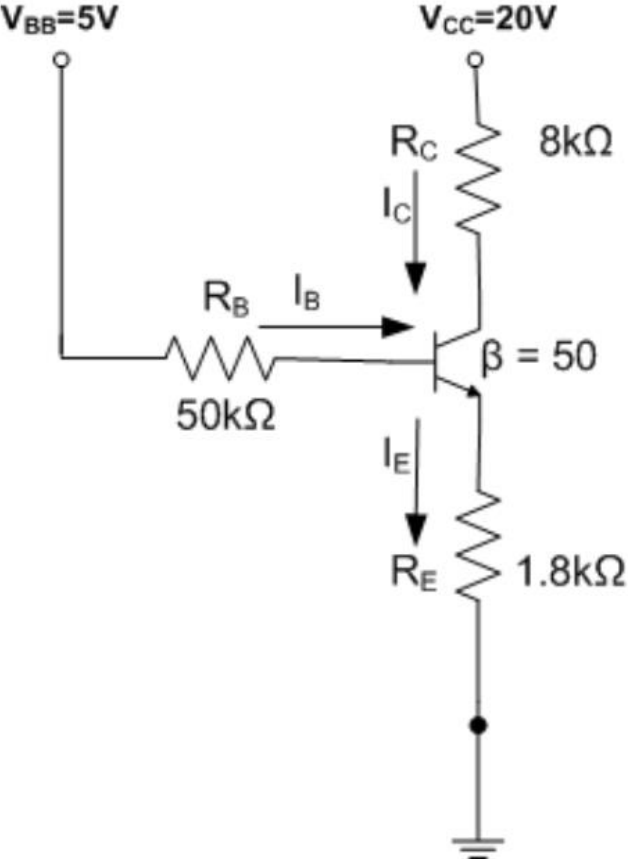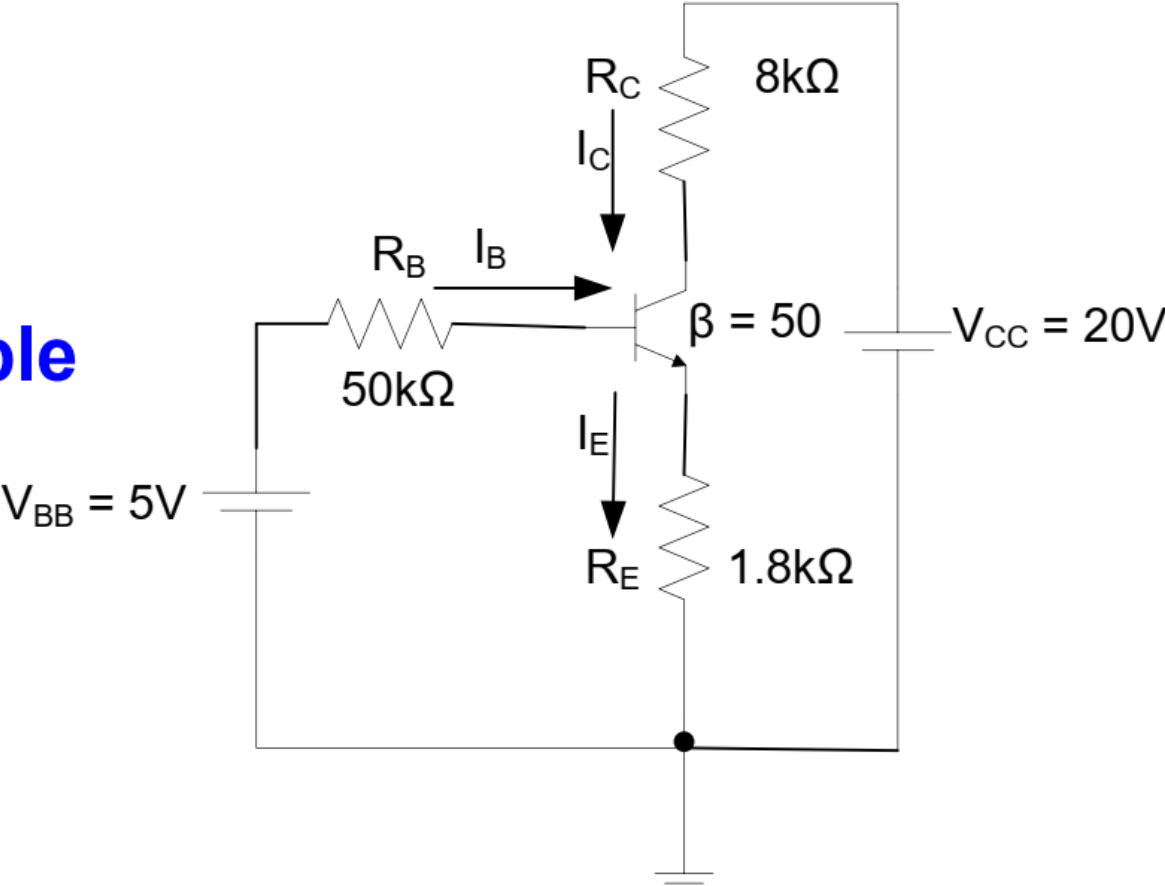

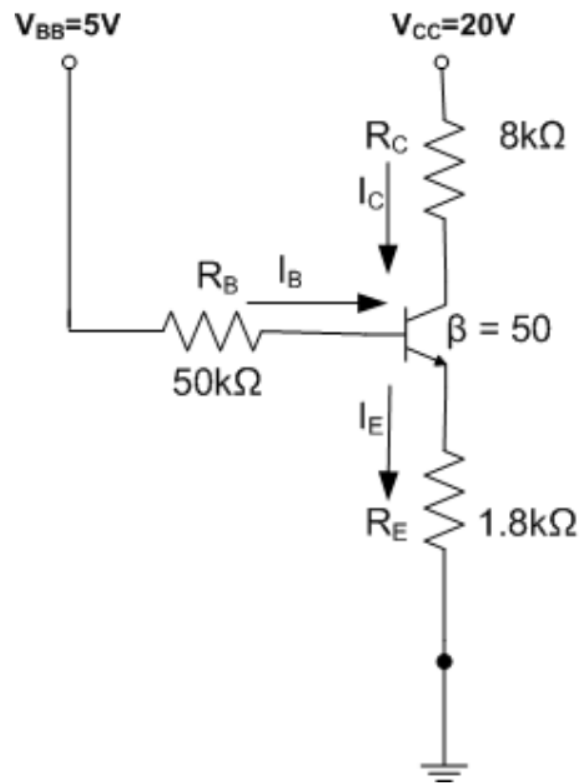

$$I_C = \beta I_B = 50 I_B \quad I_E = I_C + I_B = 51 I_B$$

$$I_B = \frac{V_{BB} - V_{BE}}{R_B + (\beta + 1)R_E} = \frac{5 - 0.7}{50 + 51 * 1.8} = 0.0303 \text{ mA}$$

$$I_C = 50 * 0.0303 = 1.52 \text{ mA} \quad I_E = 1.55 \text{ mA}$$

$$V_E = I_E R_E = 1.55 * 1.8 = 2.79 \text{ V}$$

$$V_B = V_E + V_{BE} = 2.79 + 0.7 = 3.49 \text{ V}$$


$$V_C = V_{CC} - I_C R_C = 20 - 1.52 * 8 = 7.84$$

$$V_{CE} = V_C - V_E = 7.84 - 2.79 = 5.05 \text{ V}$$

Note that $V_{BC} = 3.49 - 7.84 = -4.35 \text{ V}$, i.e. the B-C junction is reverse biased, implying that the transistor is working in the Active Mode

The Bias Point is specified by (V_{CE}, I_C, I_B)

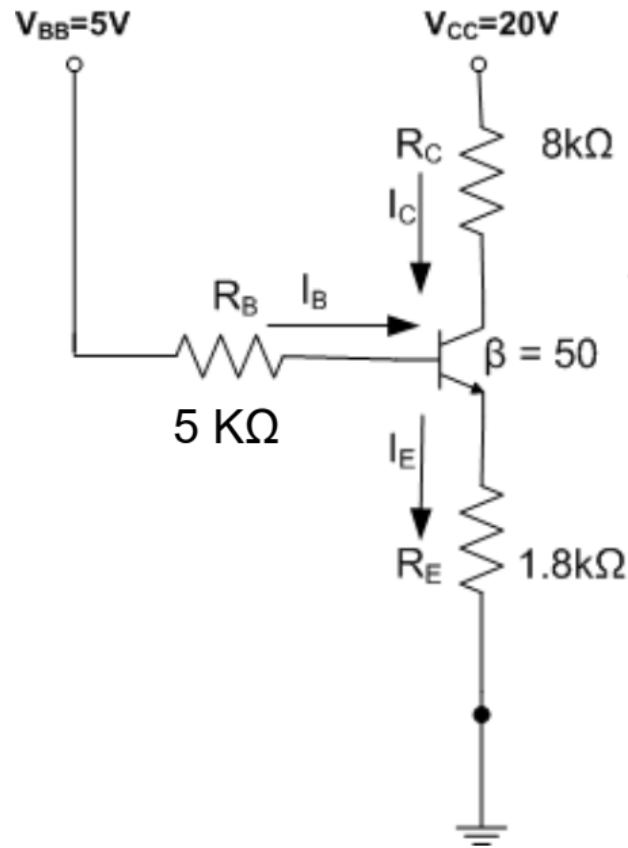What would happen if we reduced the base resistance to 5K Ω ?



Let's assume that the transistor is still in the active region so $I_C = \beta I_B$ and $I_E = (\beta + 1)I_B$. Then -

$$5 - 0.7 = 5I_B + 51I_B(1.8) \Rightarrow I_B = \frac{4.3}{5 + 51 \times 1.8} = 0.0444 \text{ mA}$$

$$I_C = 50I_B = 2.22 \text{ mA}$$


$$I_E = 51I_B = 2.2644 \text{ mA}$$

$$V_E = I_E R_E = 4.076 \text{ V}$$

$$V_B = V_E + 0.7 = 4.776 \text{ V}$$

$$V_C = V_{CC} - I_C R_C = 20 - 8I_C = 2.24 \text{ V}$$

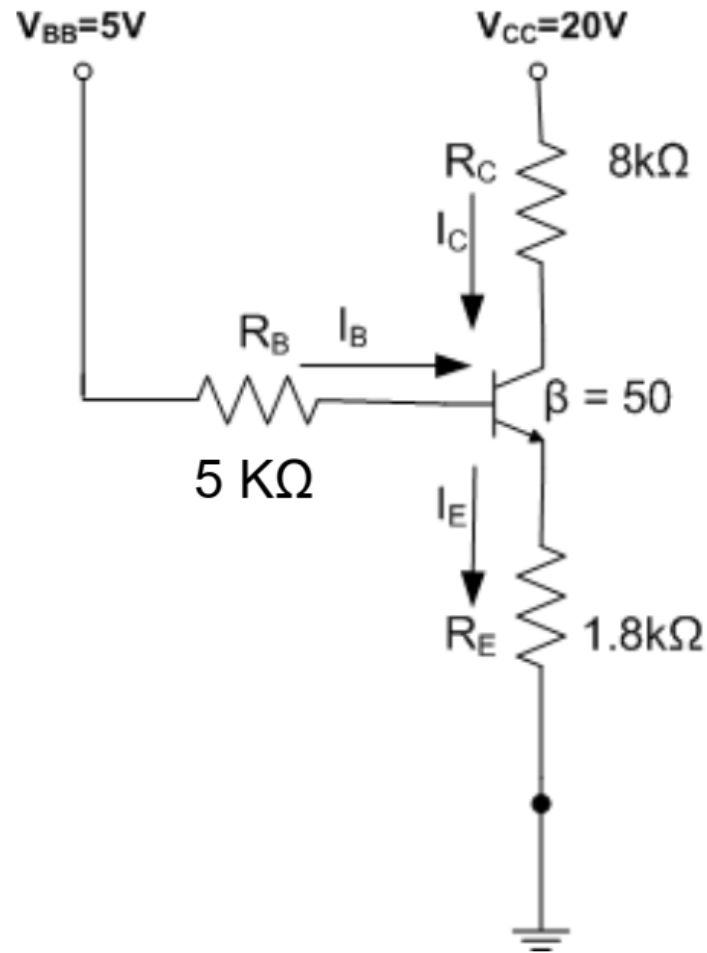
Note that B-C junction is then forward-biased which violates our earlier assumption that the transistor is in the active region. Therefore, our earlier assumption is **WRONG** – the transistor will not be in the active region



Can the transistor be in CUTOFF?

If the transistor is in CUTOFF then $I_B = I_C = I_E = 0$. Therefore $V_B = 5V$ and $V_E = 0V$ but that will forward bias B-E which violates the condition for transistor to be in CUTOFF. **Therefore, the transistor cannot be in CUTOFF.**

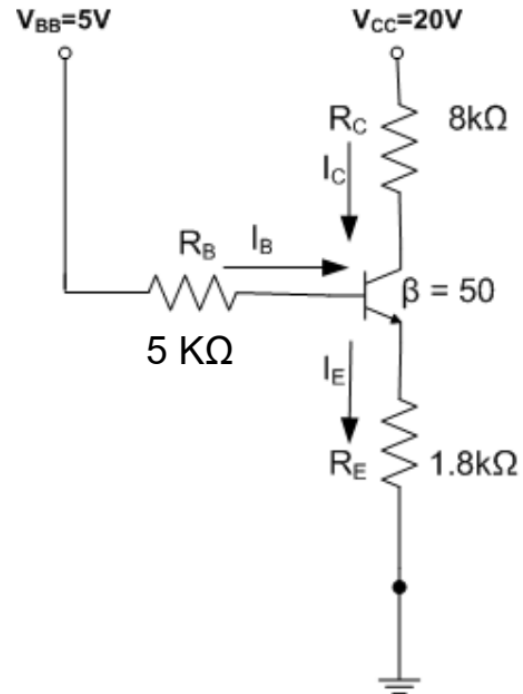What would happen if we reduced the base resistance to 5K Ω ?



Can the transistor be in Saturation?

In saturation, $V_{CE(sat)} = 0.1V$ and $V_{BE} = 0.7V$

Note that $I_C = \beta I_B$ will not hold in saturation, but we will still have $I_E = I_B + I_C$

$$+5 = 5I_B + 0.7 + 1.8(I_B + I_C) \Rightarrow 6.8I_B + 1.8I_C = 4.3$$

$$+20 = 8I_C + 0.1 + 1.8(I_B + I_C) \Rightarrow 1.8I_B + 9I_C = 19.1$$

Solving - $I_B = 0.0745 \text{ mA}$, $I_C = 2.107 \text{ mA}$ & $I_E = 2.182 \text{ mA}$

Note that

(a) $I_C < \beta I_B$

(b) $V_E = 3.93 \text{ V}$ $V_B = 4.63 \text{ V}$ $V_C = 4.03 \text{ V}$

So B-C is forward biased

The transistor is indeed in saturation


Biasing the Transistor

To operate as an amplifier a transistor must be **biased** in the active region. In that case, the transistor can amplify a ***small ac signal*** faithfully.

Bias Point (or Quiescent Operating Point, i.e. **Q-Point**) is decided by the DC voltages applied and the values of the resistances used. (See earlier example.)

The Bias Point is specified by the three quantities **V_{CE} , I_C and I_B** . *This point must be in the active region of the transistor if we want to use the transistor (with that bias point) as an amplifier.*

Biasing the Transistor

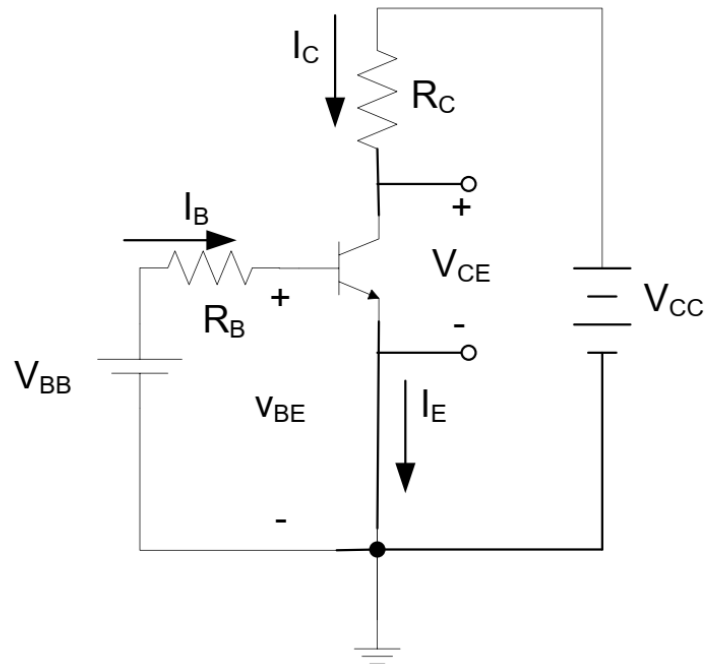

Bias Point

Intersection of the load line with the I_C - V_{CE} characteristic for the given value of I_B decides the bias point.

$$I_C = \frac{V_{CC} - V_{CE}}{R_C}$$

$$I_C = -\left(\frac{1}{R_C}\right)V_{CE} + \frac{V_{CC}}{R_C}$$

Plot of I_C vs. V_{CE} is called the 'Load Line'

