
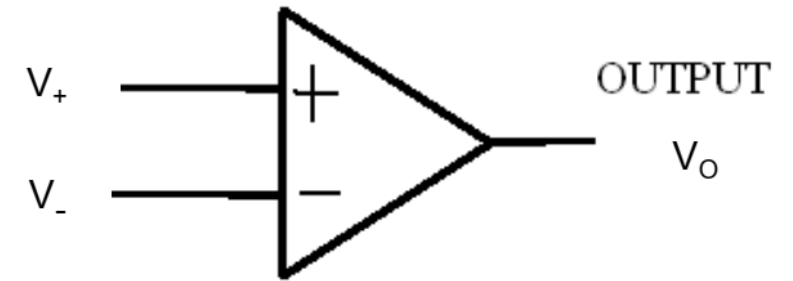


Operational Amplifier (Op- Amp)

Op-Amp Model

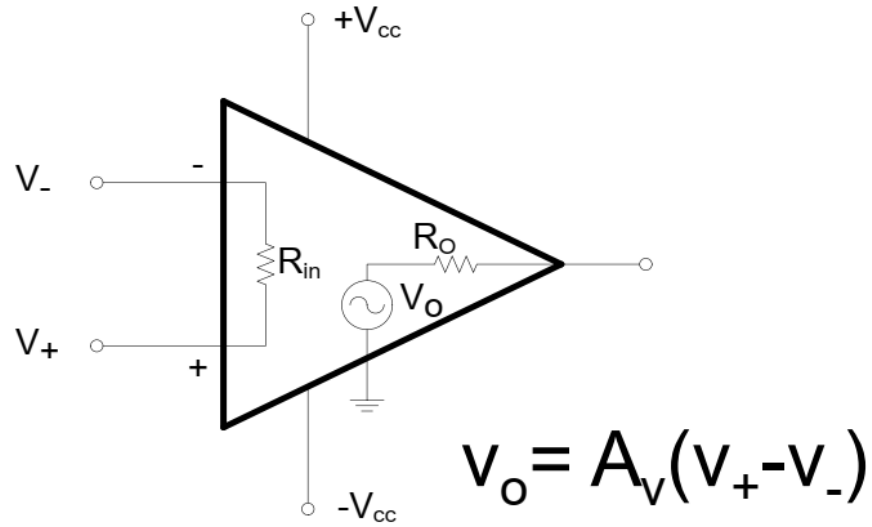

Symbol


- An Op-Amp is a very high gain amplifier
- It has high input impedance (typically a few Mega ohm)

It has a low output impedance (less than 100Ω)

Characteristics of an ideal OP-Amp

- Input Resistance $R_i = \infty$
- Output Resistance $R_o = 0$
- Voltage Gain $A_v = \infty$
- Bandwidth = ∞ (i.e. can work over a wide range of frequencies)
- Perfect balance i.e $v_o = 0$ when $v_1 = v_2$
- Characteristics do not drift with temperature

Ideal Op-Amp analysis

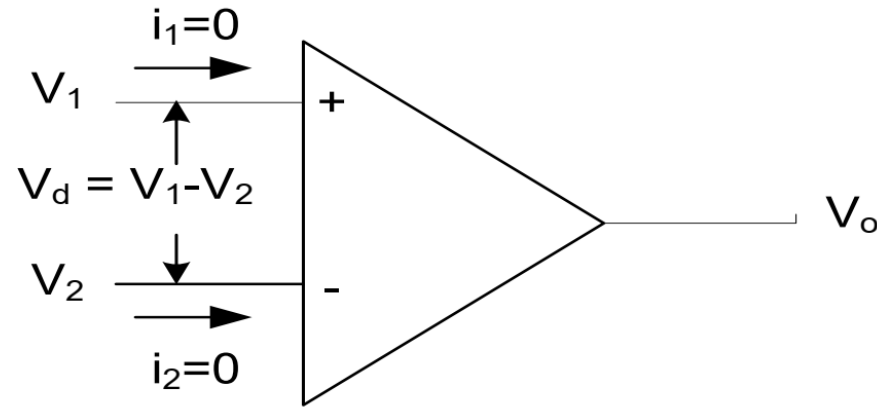

i) $R_i = \infty$,

No current enters into op-amp

Voltage Gain $A_v = \infty$ or, $v_o / v_d = \infty$


or, $v_d = v_o / \infty = 0$ [since v_o is finite]

Therefore, $v_1 - v_2 = 0$

or,

ii) **$v_1 = v_2$**

1. Inverting Amplifier

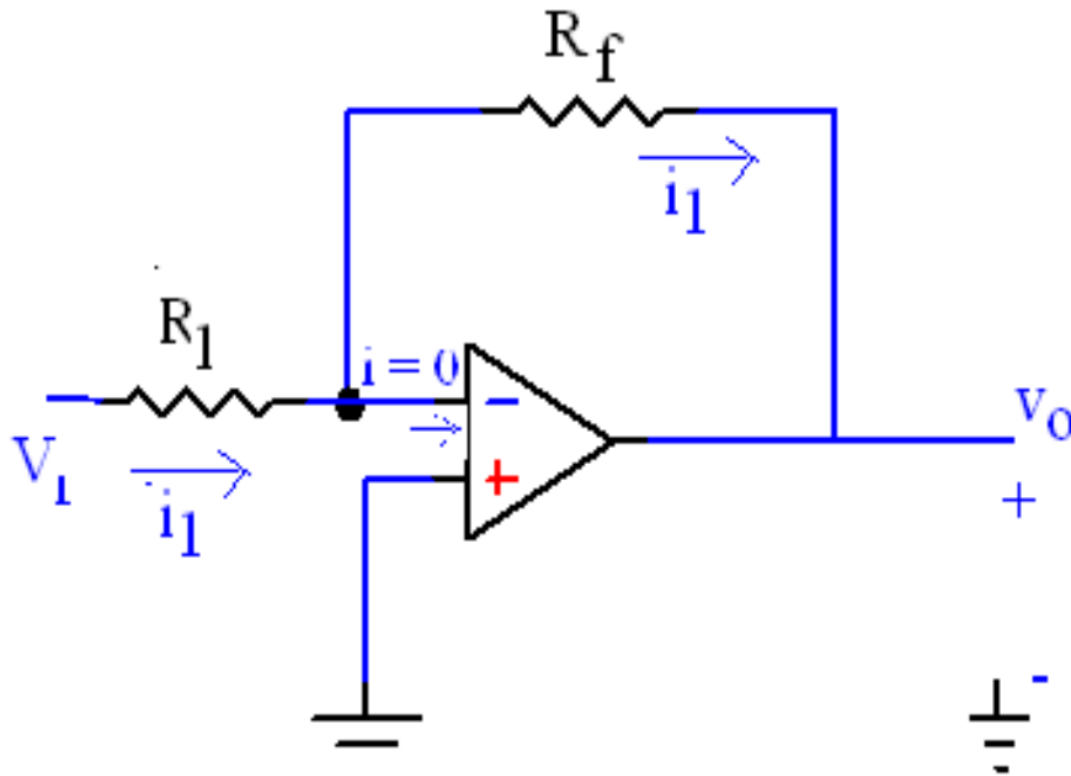

The (-) terminal is effectively at ground. This is referred to as “**Virtual Ground**”

Using KVL,

$$v_1 - i_1 R_1 = 0$$

$$\Rightarrow i_1 = v_1 / R_1$$

&

$$0 - i_1 R_f - v_o = 0$$

$$\text{or, } v_o = -i_1 R_f = -v_1 R_f / R_1$$

$$v_o / v_1 = -R_f / R_1$$

2. Non Inverting Amplifier


$$v_- = v_+ = v_1$$

$$i = \frac{v_1}{R_1} = \frac{v_o - v_1}{R_f}$$


$$v_o = R_f \left[\frac{1}{R_1} + \frac{1}{R_f} \right] v_1$$

Gain
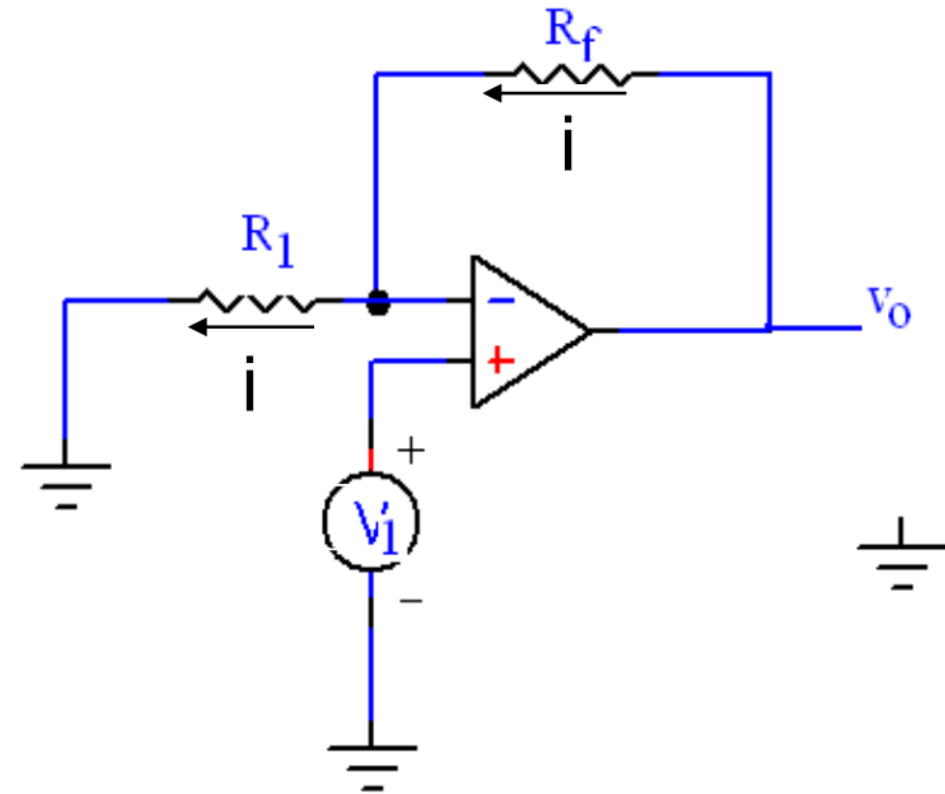
$$\frac{v_o}{v_1} = \left(1 + \frac{R_f}{R_1} \right)$$



3. Voltage Follower

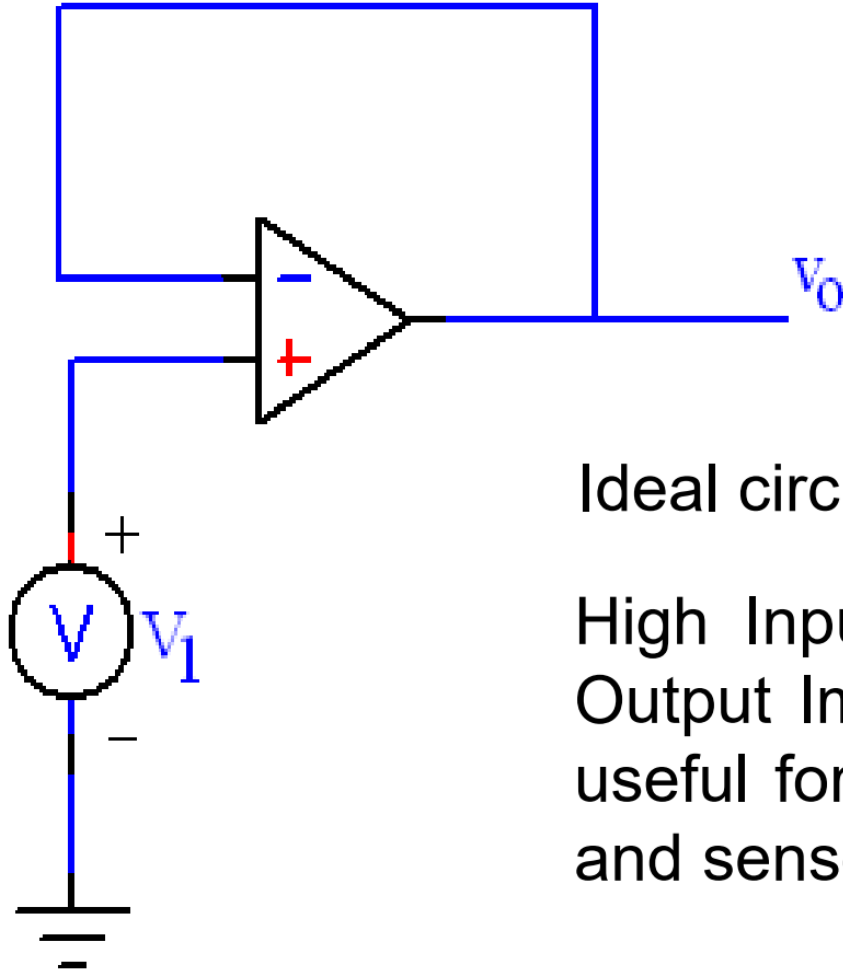

$$V_o = V_1$$


Ideal circuit to test Op-Amp

High Input Impedance and Low Output Impedance also makes it useful for interfacing transducers and sensors to other circuits

4. Summing Amplifier

Use superposition
(i.e. consider one
source at a time and
add their respective
outputs)

Can also be done
directly

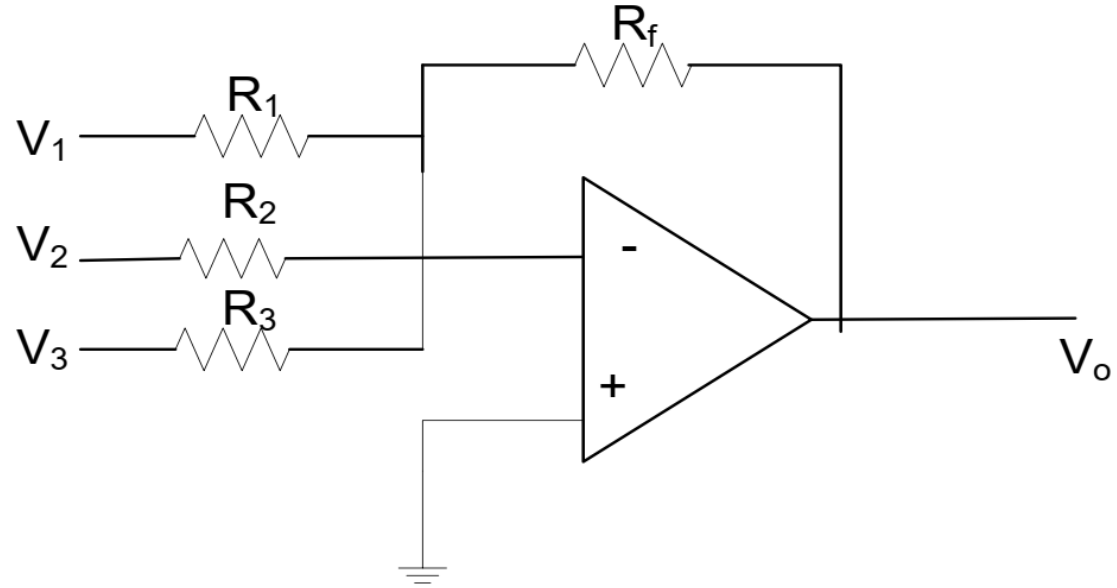

$$v_o = - \left[\frac{R_f}{R_1} v_1 + \frac{R_f}{R_2} v_2 + \frac{R_f}{R_3} v_3 \right]$$

Difference Amplifier (or Voltage Subtractor)

Use Superposition


(can also be done directly)

$$\text{If } v_2=0, \quad v_{o1} = -\frac{R_2}{R_1} v_1$$

$$\begin{aligned} \text{If } v_1=0, \quad v_{o2} &= v_2 \left[\frac{R_2}{R_1 + R_2} \right] \left[1 + \frac{R_2}{R_1} \right] \\ &= v_2 \frac{R_2}{R_1} \end{aligned}$$

$$\text{Therefore,} \quad v_o = v_{o1} + v_{o2} = \frac{R_2}{R_1} (v_2 - v_1)$$

$$\text{Difference Gain} = R_2/R_1$$

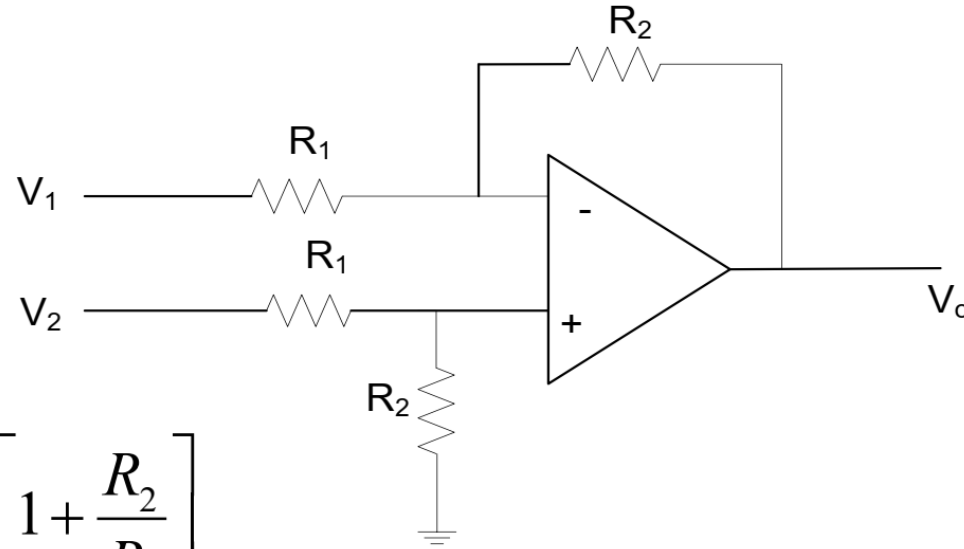

Instrumentation Amplifier

$$V_B = V_1 \quad V_C = V_2$$

$$\frac{V_D - V_2}{R_1} = \frac{V_2 - V_1}{R_{gain}} \Rightarrow V_D = V_2 + \frac{R_1}{R_{gain}}(V_2 - V_1)$$

$$\text{Similarly, } V_A = V_1 - \frac{R_1}{R_{gain}}(V_2 - V_1)$$


$$V_F = \left(\frac{R_3}{R_2 + R_3} \right) V_D = V_E$$

$$\frac{V_{out} - V_E}{R_3} = \frac{V_E - V_A}{R_2} \Rightarrow V_{out} = \left(1 + \frac{R_3}{R_2} \right) V_E - \frac{R_3}{R_2} V_A$$

$$V_{out} = \frac{R_3}{R_2} (V_D - V_A) = \left(1 + \frac{2R_1}{R_{gain}} \right) \left(\frac{R_3}{R_2} \right) (V_2 - V_1)$$

$$\frac{V_{out}}{V_2 - V_1} = \left(1 + \frac{2R_1}{R_{gain}} \right) \frac{R_3}{R_2}$$

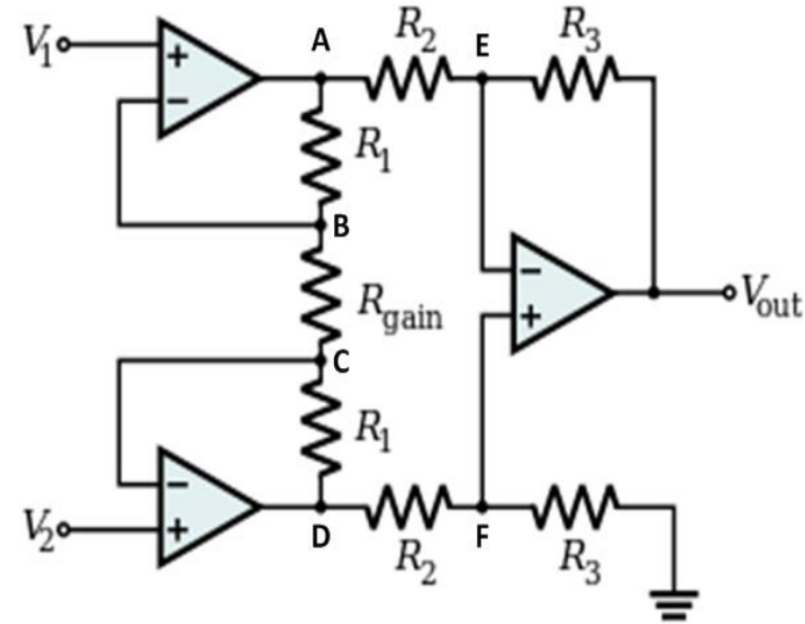Gain can be varied by just changing one resistor, R_{gain}




Integrator

$$i = \frac{v_1}{R} \quad v_o = -\frac{1}{C} \int_0^t i dt \quad \text{with } v_o(0) = 0$$

Therefore,
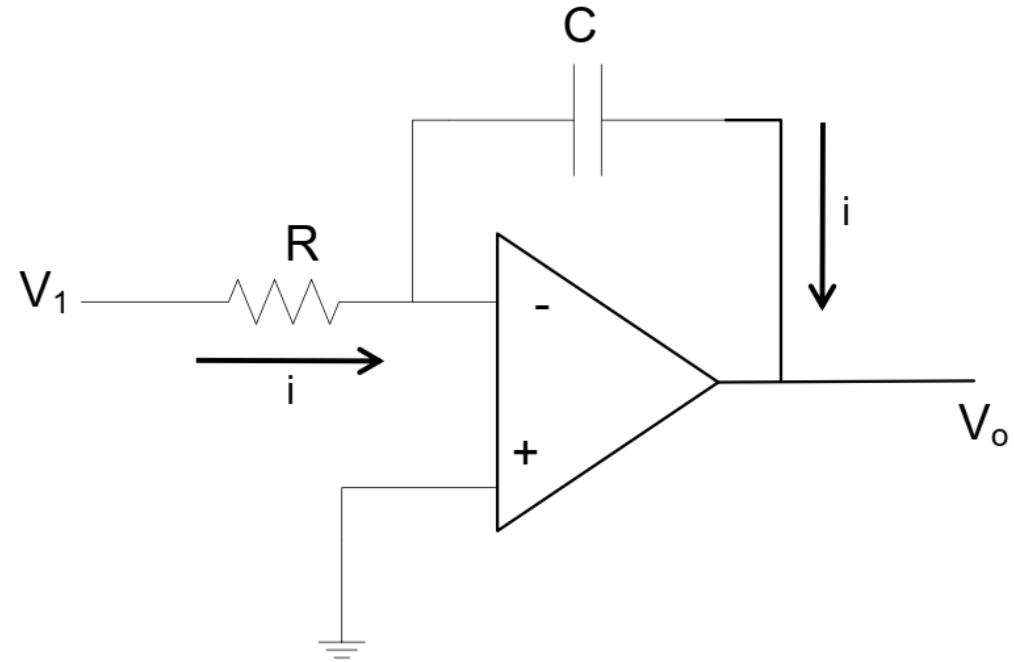
$$v_o = -\frac{1}{RC} \int_0^t v_1 dt \quad \text{with } v_o(0) = 0$$



v_o

Differentiator

$$v_1 = \frac{1}{C} \int_0^t i dt \quad \text{with } v_1(0) = 0$$


$$v_o = -iR$$

Therefore,

$$v_1 = -\frac{1}{RC} \int_0^t v_o dt$$


or

$$v_o = -RC \frac{dv_1}{dt}$$

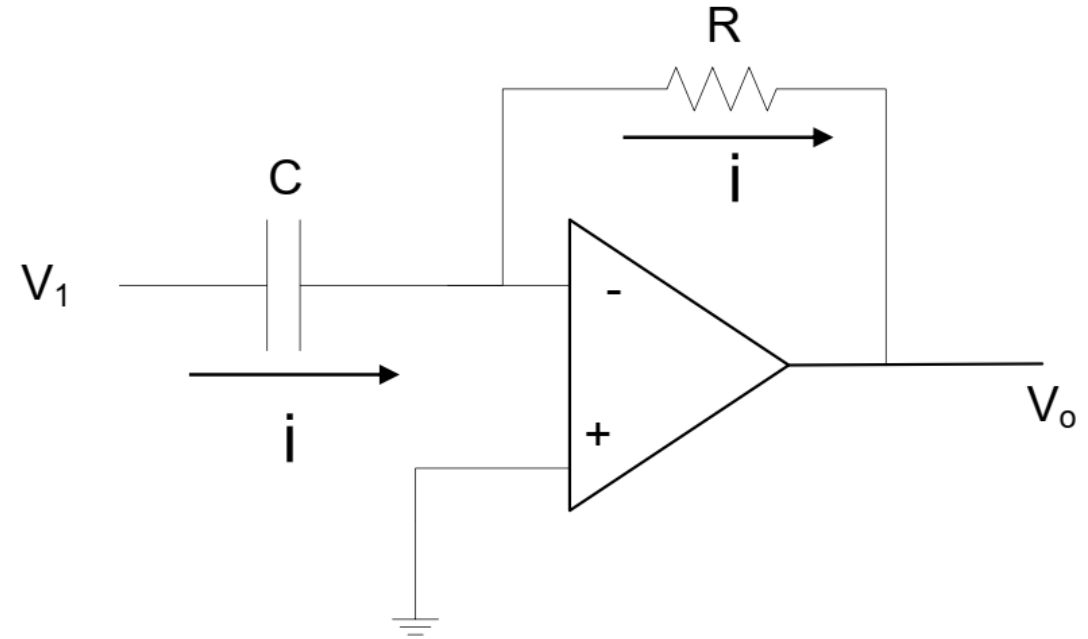

Example

Find v_o in the given circuit.

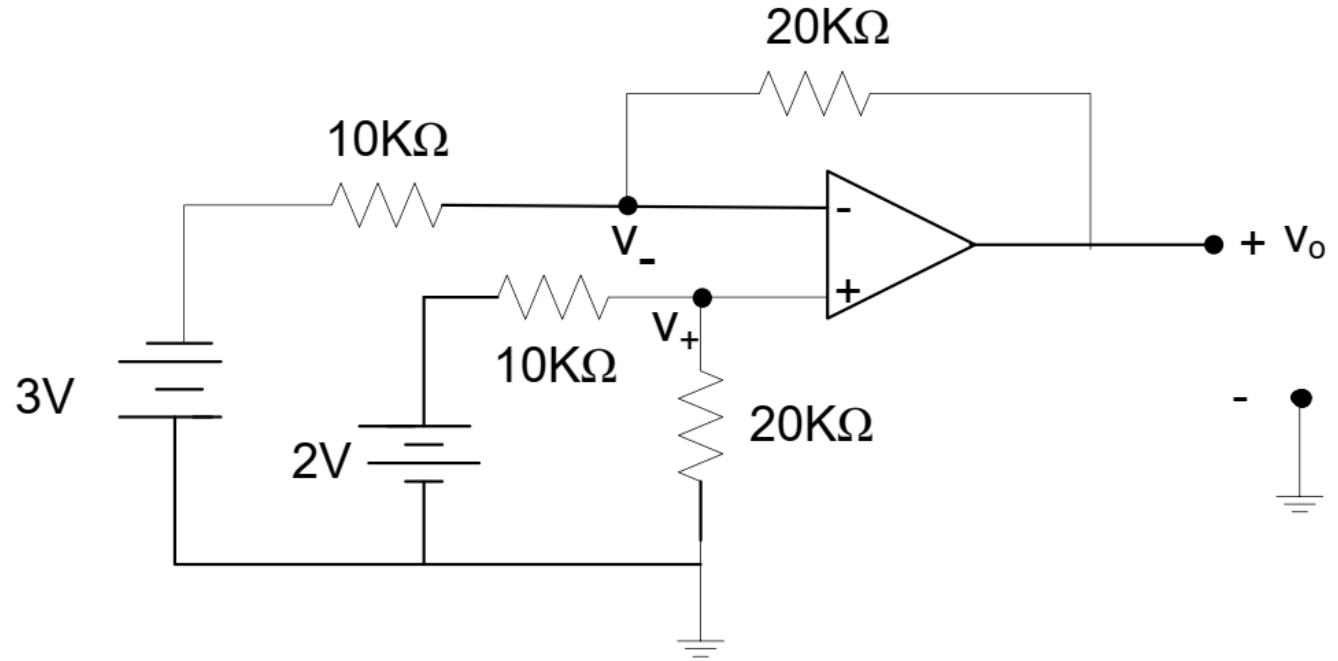

$$v_- = v_+ = 2 \times \frac{20}{30} = \frac{4}{3}$$

$$\frac{v_o - v_-}{20} = \frac{v_- - (-3)}{10}$$

$$\frac{v_o}{20} = v_- \left(\frac{1}{10} + \frac{1}{20} \right) + \frac{3}{10}$$

$$v_o = 3v_- + 6 = 10 \text{ V}$$

Example


Find the gain v_o/v_i in the given circuit.

$$v_- = v_+ = 0 \quad \text{Virtual Ground at } (-)$$

$$\frac{v_i}{R_1} = -\frac{v}{R} \quad \Rightarrow \quad v = -\frac{R}{R_1} v_i$$

$$\frac{v_o - v}{R_2} = \frac{v}{R} + \frac{v}{R} = \frac{2v}{R}$$
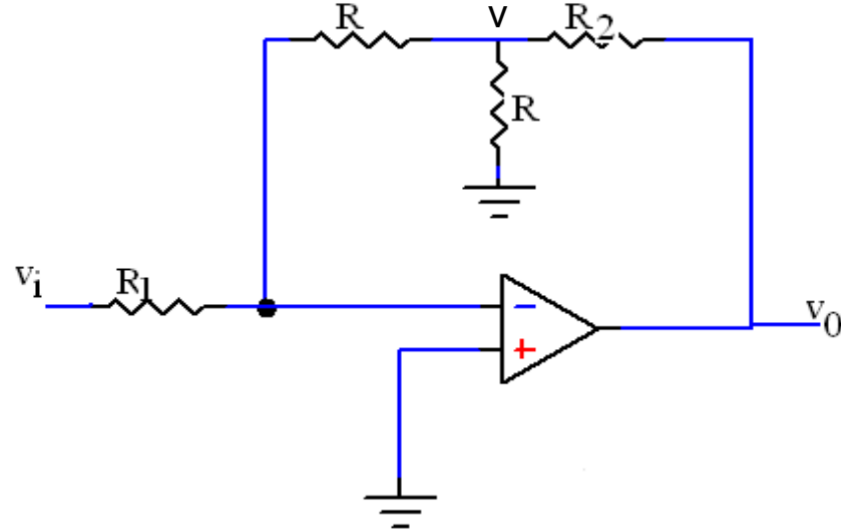
$$\begin{aligned} v_o &= v \left[1 + \frac{2R_2}{R} \right] \\ &= -\left[\frac{R}{R_1} \right] \left[1 + \frac{2R_2}{R} \right] v_i \end{aligned}$$



Gain

$$A_v = \frac{v_o}{v_i} = -\left(\frac{R + 2R_2}{R_1} \right)$$

$$i_1 = \frac{v - v_{IN}}{2R} = \frac{v_O - v}{2R} \Rightarrow 2v - v_O = v_{IN}$$

$$i_2 = \frac{v}{2R} = \frac{v_L - v}{R} \Rightarrow v_L = \frac{3}{2}v$$

$$i_L = \frac{v_O - v_L}{R} - \frac{v_L - v}{R} = \frac{v_O - 3v + v}{R} = \frac{v_O - 2v}{R}$$

Therefore, $i_L = -\frac{v_{IN}}{R}$

