

Department of Electronics and Electrical Engineering
Indian Institute of Technology Guwahati

EE101 - Basic Electronics

Pre-Tutorial Assignment 1: Solutions

1. Apply Ohm's Law, KCL and KVL to evaluate i_x and V_x from the circuit shown in Figure 1.

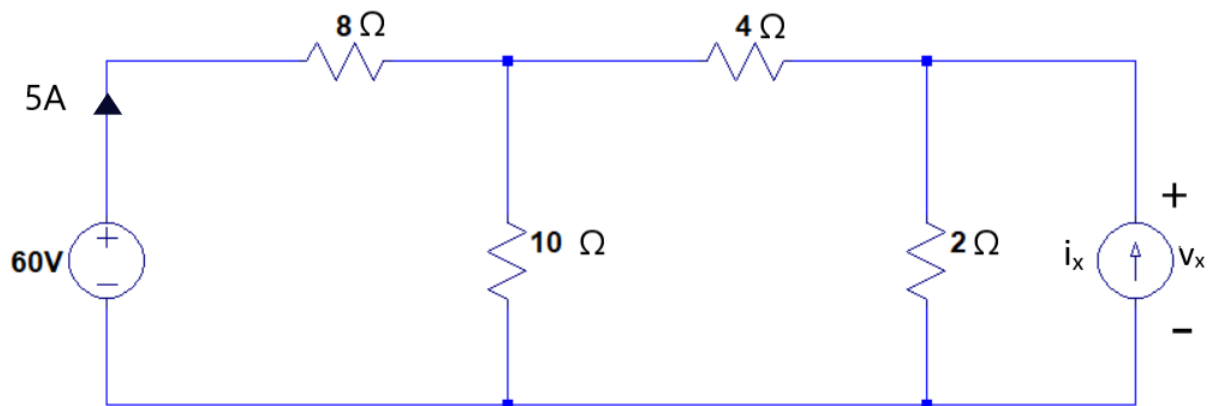


Figure 1: Evaluate i_x and v_x from the above circuit.

Solution

Figure 1 shows the different branch voltages and currents with their respective polarities and directions. The nodes are marked as A , B , C and D

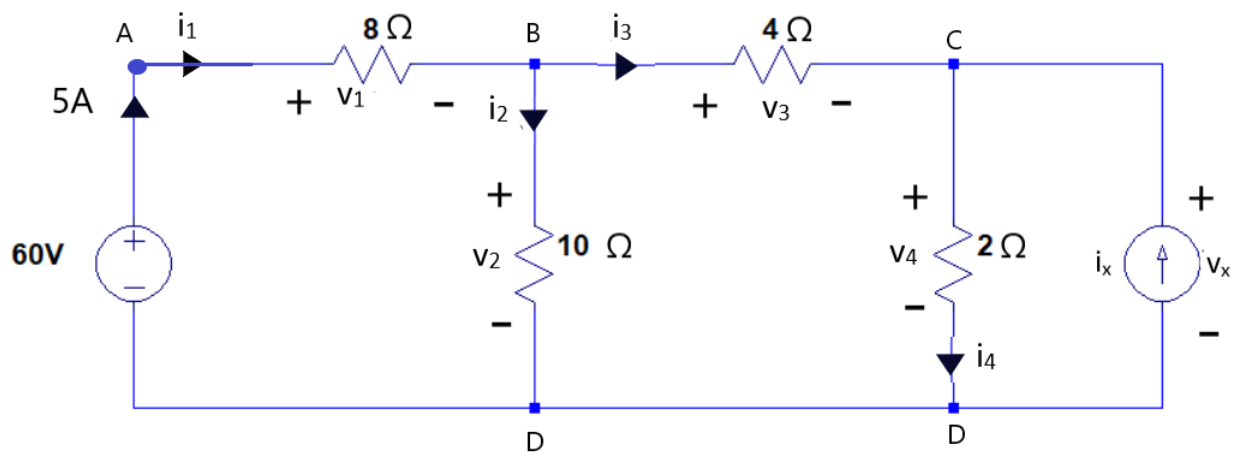


Figure 2: Branch voltages and currents are shown with their respective polarities and directions.

Apply KCL at node A: $i_1 = 5A$

$$\Rightarrow V_1 = 8\Omega \times 5A$$

$$\Rightarrow V_1 = 40 \text{ V}$$

Apply KVL : A-B-D-A (Voltage drop taken positive)

$$V_1 + V_2 - 60 = 0$$

$$\Rightarrow V_2 = 60 - V_1$$

$$\Rightarrow V_2 = 20 \text{ V}$$

$$\Rightarrow i_2 = \frac{20 \text{ V}}{10 \Omega}$$

$$\Rightarrow i_2 = 2 \text{ A}$$

Apply KCL at Node B : $i_1 = i_2 + i_3$

$$\Rightarrow i_3 = 5 - 2$$

$$\Rightarrow i_3 = 3 \text{ A}$$

$$\Rightarrow V_3 = 3 \text{ A} * 4 \Omega$$

$$\Rightarrow V_3 = 12 \text{ V}$$

Apply KVL : B-C-D-B (Voltage drop taken positive)

$$V_3 + V_4 - V_2 = 0$$

$$\Rightarrow V_4 = 20 - 12$$

$$\Rightarrow V_4 = 8 \text{ V}$$

$$\Rightarrow i_4 = \frac{8 \text{ V}}{2 \Omega} = 4 \text{ A}$$

Hence, $V_x = 8 \text{ V}$

Apply KCL at Node C : $i_3 + i_x = i_4$

$$\Rightarrow i_x = 4 - 3$$

Hence, $i_x = 1 \text{ A}$

2. For each of the two circuits given below, compute the truth table for the output in terms of the inputs. Does the tables look familiar?


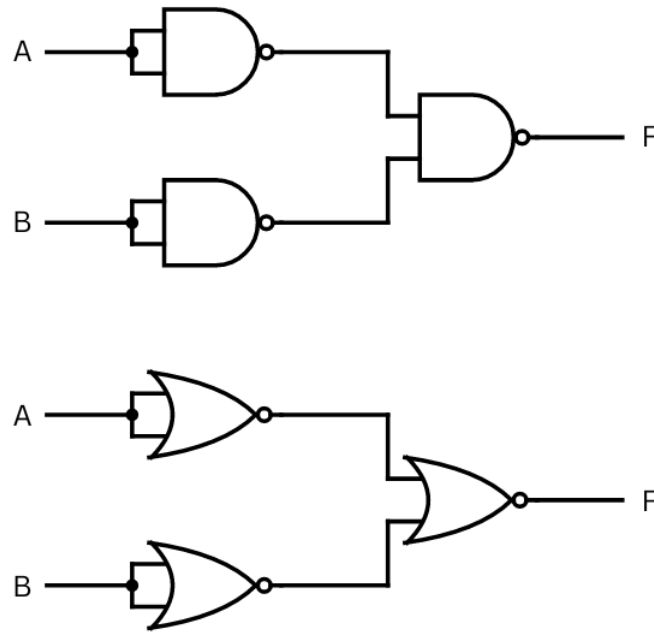


Figure 3: A logic gate circuit

Solution

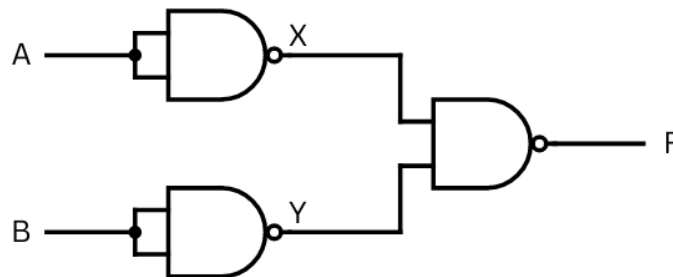Consider the variables X and Y shown below. Using the truth table of the 2-input NAND gate, we can compute what the values of X and Y are as a function of the inputs A and B .




The truth table for F can be obtained as follows:

A	B	X	Y	F
0	0	1	1	0
0	1	1	0	1
1	0	0	1	1
1	1	0	0	1

The circuit can be recognized as the OR Gate from the truth table.

Consider the variables X and Y shown below. Using the truth table of the 2-input NOR gate, we can compute what the values of X and Y are as a function of the inputs A and B .

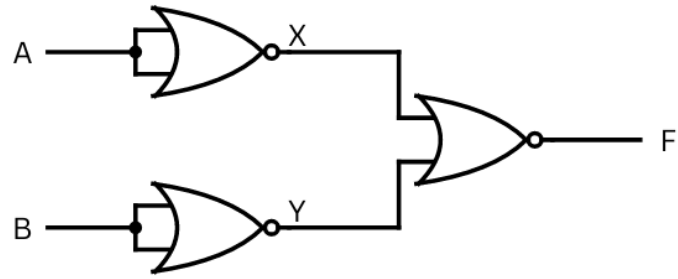The truth table for F can be obtained as follows:



A	B	X	Y	F
0	0	1	1	0
0	1	1	0	0
1	0	0	1	0
1	1	0	0	1

The circuit can be recognized as the AND Gate from the truth table.