

Indian Institute of Technology Guwahati
Department of Electronics and Electrical Engineering
EE101 - Basic Electronics

Pre-Tutorial Assignment - 1

Date: Aug 10, 2023

Marks: 2

1. Apply Ohm's Law, KCL and KVL to evaluate i_x and V_x from the circuit shown in Figure 2.

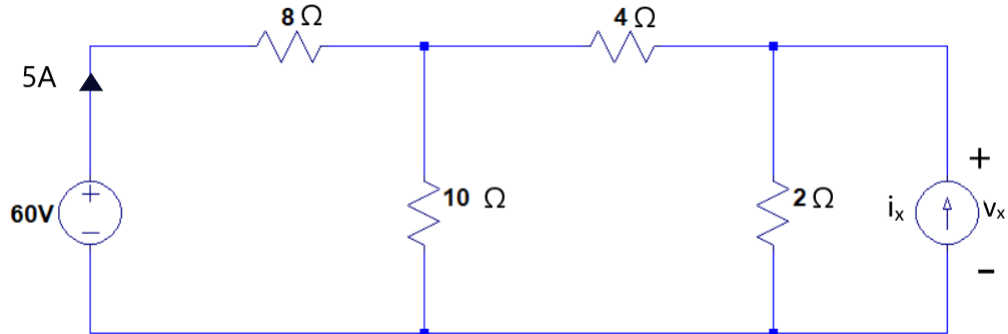


Figure 1: Evaluate i_x and v_x from the above circuit.

2. For each of the two circuits given below, compute the truth table for the output in terms of the input. Does the tables look familiar?

