

Department of Electronics and Electrical Engineering
Indian Institute of Technology Guwahati

EE101 - Basic Electronics

Pre-Tutorial Assignment 4: Solutions

1. Consider the electric circuit shown in Figure 1. The circuit elements have the following numerical values – $R_1 = 20\Omega$, $R_2 = 10\Omega$, $R_3 = 30\Omega$, $I_1 = 4A$, $V_1 = 60V$, $I_d = k \times i = 0.4 \times i$. Evaluate the voltage V_{R3} across the resistor R_3 using the *Superposition Theorem*. Report the numerical values of $V_{R3}(I_1)$ (when only I_1 is active) and $V_{R3}(V_1)$ (when only V_1 is active).

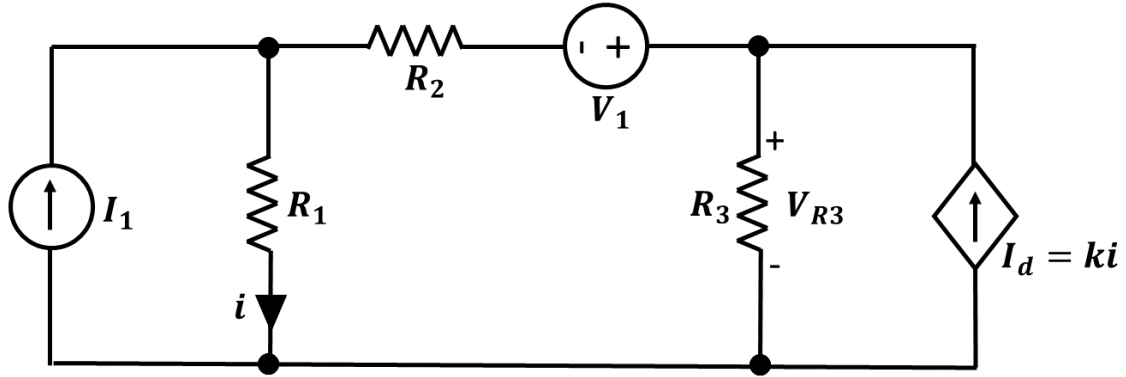


Figure 1: Electric circuit with two independent sources and one dependent source.

Solution

The voltage V_{R3} across the resistor R_3 can be obtained by adding the voltages measured in two individual circuits, each having one active independent source. Thus, by using the Superposition theorem, $V_{R3} = V_{R3}(I_1) + V_{R3}(V_1)$

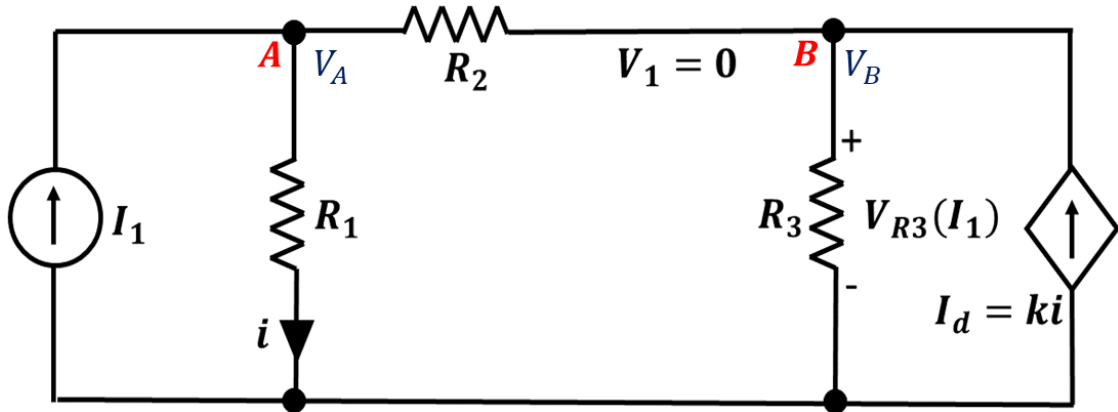


Figure 2: The independent voltage source is deactivated and only the current source I_1 is active.

Figure 2 shows the circuit with only source I_1 active. Application of KCL at Node **A** gives us

$$I_1 - G_1 V_A - G_2 (V_A - V_B) = 0 \quad (1)$$

$$\Rightarrow (G_1 + G_2) V_A - G_2 V_B = I_1 \quad (2)$$

Application of KCL at Node **B** gives us

$$G_2(V_A - V_B) - G_3V_B + I_d = 0 \quad (3)$$

$$\Rightarrow -(kG_1 + G_2)V_A + (G_2 + G_3)V_B = 0 \quad (4)$$

Using the numerical values and by solving equations 2 and 4, we obtain $V_{R3}(I_1) = V_B = 60V$

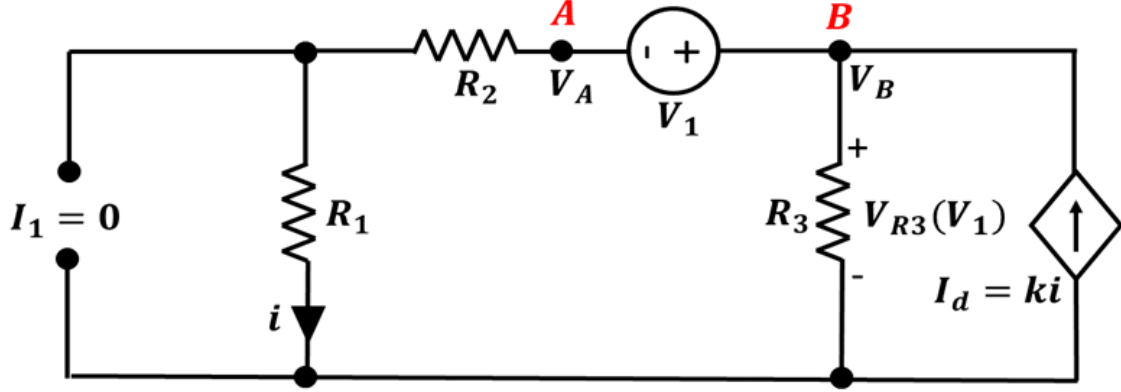


Figure 3: The independent current source is deactivated and only the voltage source V_1 is active.

Figure ?? shows the circuit with only source V_1 active. Application of KCL at Node **B** and an inspection of the circuit gives us the following equations.

$$-i - G_3V_B + I_d = 0 \quad (5)$$

$$i = \frac{V_A}{R_1 + R_2} \quad (6)$$

$$V_B - V_A = V_1 \quad (7)$$

$$(8)$$

Using the above equations, we obtain the following

$$\frac{(k-1)(V_B - V_1)}{R_1 + R_2} = G_3V_B \quad (9)$$

$$\Rightarrow V_B = \frac{\alpha V_1}{\alpha - G_3} \quad (10)$$

$$(11)$$

where $\alpha = \frac{k-1}{R_1 + R_2}$. Using the numerical values, we obtain $V_{R3}(V_1) = 22.5V$

Thus, using the Superposition theorem, we obtain $V_{R3} = V_{R3}(I_1) + V_{R3}(V_1) = 82.5V$

2. Consider the Boolean function

$$F(A, B, C) = \Sigma(0, 1, 2, 5, 6, 7).$$

- (a) Draw the Karnaugh map for the function F .
- (b) Find all the Boolean expressions for F in the minimal SOP form.
- (c) Find all the Boolean expressions for F in the minimal POS form.

Solution

- (a) The K-map for the function F is

		BC			
		00	01	11	10
A	0	1	1	0	1
	1	0	1	1	1

- (b) In the K-map above, each 1 can be covered by two groupings of 1's as shown below. Thus the

		BC			
		00	01	11	10
A	0	1	1	0	1
	1	0	1	1	1

minimal SOP expressions may not be unique. The minimal SOP expressions can be found by considering the following coverings:

		BC			
		00	01	11	10
A	0	1	1	0	1
	1	0	1	1	1

$$F(A, B, C) = \overline{A}.\overline{B} + A.C + B.\overline{C}$$

BC		00	01	11	10
A	0	1	1	0	1
	1	0	1	1	1

$$F(A, B, C) = \overline{A}.\overline{B} + A.C + B.\overline{C}$$

(c) In the K-map above, we can consider the coverings of 0's as shown below. The unique minimal

BC		00	01	11	10
A	0	1	1	0	1
	1	0	1	1	1

POS expression is

$$(\overline{A} + B + C).(A + \overline{B} + \overline{C})$$