

Department of Electronics and Electrical Engineering
Indian Institute of Technology Guwahati

EE101 - Basic Electronics

Date: Sep 6, 2023

Pre-Tutorial Assignment 5

Marks: 2

1. A linear network $\mathbf{N}$ (with unique solution) delivers $3.5A$ when the load connected is 5.25Ω and $2.1A$ when the load is 19.5Ω . What is the maximum power $P_{max}(\mathbf{N})$ (in W) that $\mathbf{N}$ can deliver?
2. Consider an Excess-3 to BCD code converter. Let the Excess 3 input be represented by four bits $PQRS$ and the BCD output be represented by four bits $ABCD$.
 - (a) Draw the K-maps for A and B
 - (b) Find a Boolean expression for A in the minimal SOP form.
 - (c) Find a Boolean expression for B in the minimal POS form.