

Indian Institute of Technology Guwahati
Department of Electronics and Electrical Engineering
EE101 - Basic Electronics

Tutorial - 9

Date: Oct 19, 2023

1. For the emitter-bias network in the active region (base-emitter forward bias, base-collector reverse bias) Fig.1, let $V_{CC} = +18V$, $\beta = 60$, $R_B = 430k\Omega$, $R_C = 2k\Omega$, $R_E = 1k\Omega$. Determine the following (assume $V_{BE} = 0.7V$):

- (a) I_B
- (b) I_C
- (c) V_{CE}
- (d) V_C
- (e) V_E
- (f) V_B
- (g) V_{BC}

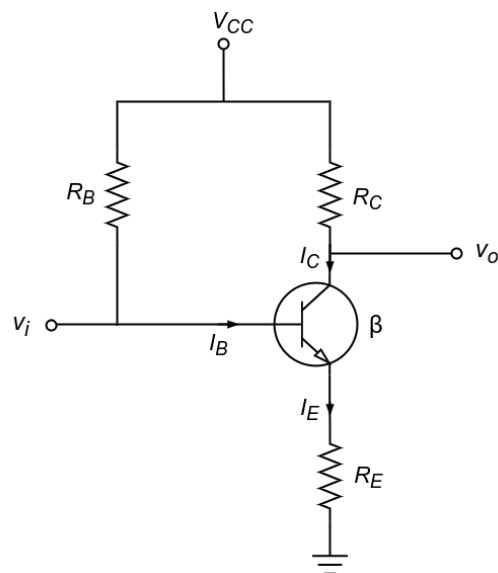


Figure 1

Solution :

(a)

$$\begin{aligned} I_B &= \frac{V_{CC} - V_{BE}}{R_B + (\beta + 1)R_E} \\ &= \frac{18 - 0.7}{430k\Omega + (61)(1k\Omega)} \\ &= \frac{17.3}{491} \\ &= 35.23\mu A \end{aligned}$$

(b)

$$\begin{aligned} I_C &= \beta I_B \\ &= (60)(35.23\mu A) \\ &= 2.11mA \end{aligned}$$

(c)

$$\begin{aligned}I_E &= (\beta + 1)I_B \\&= (61)(35.23\mu A) \\&= 2.15mA\end{aligned}$$

$$\begin{aligned}V_{CE} &= V_{CC} - I_C R_C - I_E R_E \\&= 18V - (2.11mA * 2k\Omega) - (2.15mA * 1k\Omega) \\&= 18V - 6.37V \\&= 11.63V\end{aligned}$$

(d)

$$\begin{aligned}V_C &= V_{CC} - I_C R_C \\&= 18V - (2.11mA)(2k\Omega) \\&= 18V - 4.22V \\&= 13.78V\end{aligned}$$

(e)

$$\begin{aligned}V_E &= V_C - V_{CE} \\&= 13.78V - 11.63V \\&= 2.15V\end{aligned}$$

or

$$\begin{aligned}V_E &= I_E R_E \\&= (2.15mA)(1k\Omega) \\&= 2.15V\end{aligned}$$

(f)

$$\begin{aligned}V_B &= V_{BE} + V_E \\&= 0.7V + 2.15V \\&= 2.85V\end{aligned}$$

(g)

$$\begin{aligned}V_{BC} &= V_B - V_C \\&= 2.85V - 13.78V \\&= -10.93V\end{aligned}$$

2. Determine the region where the transistor is operating. Accordingly, compute the base current and the collector current. Let $V_{CC} = 10V$, $V_{BB} = 5V$, $R_C = 12k\Omega$, $R_B = 50k\Omega$, $R_E = 5k\Omega$. Assuming $\beta = 60$, $V_{BE} = 0.7V$ and V_{CE} at saturation is $0.1V$

Solution

Assume the transistor is in the active region.

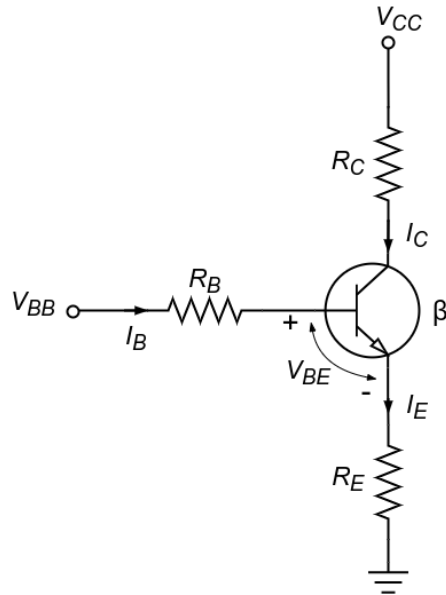


Figure 2

$$\begin{aligned}
 I_B &= \frac{V_B - V_{BE}}{R_B + (\beta + 1)R_E} \\
 &= \frac{5 - 0.7}{50 + 5(61)} \\
 &= 12.11 \mu A
 \end{aligned}$$

$$\begin{aligned}
 I_C &= \beta I_B \\
 &= 60 * 12.11 \\
 &= 0.726 mA
 \end{aligned}$$

$$\begin{aligned}
 V_C &= V_{CC} - I_C R_C \\
 &= 10 - 0.726 * 12 \\
 &= 1.28 V
 \end{aligned}$$

$$\begin{aligned}
 V_B &= V_{BB} - I_B R_B \\
 &= 5 - 12.11 * 50 \\
 &= 5 - 0.605 \\
 &= 4.39 V
 \end{aligned}$$

Since $V_{CB} < 0$, the transistor is not in the active region. Instead, it is in the saturation region.

Base-Emitter Loop

$$\begin{aligned}
 5 &= 50I_B + 0.7 + 5(I_B + I_C) \\
 55I_B + 5I_C &= 4.3
 \end{aligned}$$

Collector-Emitter Loop

$$\begin{aligned}
 10 &= 12I_C + 0.1 + 5(I_C + I_B) \\
 5I_B + 17I_C &= 9.9
 \end{aligned}$$

Solving for I_B and I_C , we get

$$\begin{aligned}
 I_B &= 25.93 \mu A \\
 I_C &= 0.57 mA
 \end{aligned}$$

3. Calculate the line currents in the three-wire $Y - Y$ system of Figure 3.

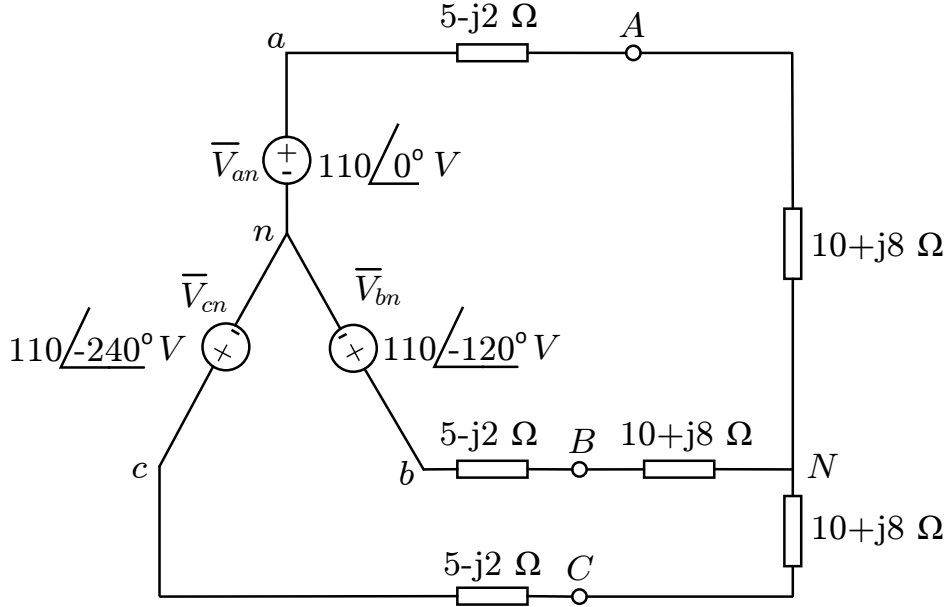


Figure 3 Three-wire $Y - Y$ system.

Solution

Note: $\bar{\text{bar}}$ indicates phasor quantity.

The three-phase circuit in Figure 3 is balanced. We may replace it with its single-phase equivalent circuit.

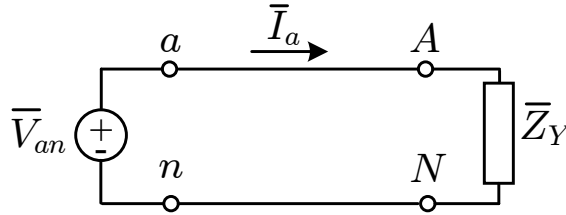


Figure 4 Single-phase equivalent circuit.

We obtain $\bar{I}_a$ from the single-phase analysis as

$$\bar{I}_a = \frac{\bar{V}_{an}}{\bar{Z}_Y}$$

where, $\bar{Z}_Y = (5 - j2) + (10 + j8) = 15 + j6 = 16.155\angle 21.8^\circ$. Hence,

$$\bar{I}_a = \frac{110\angle 0^\circ}{16.155\angle 21.8^\circ} = 6.81\angle -21.8^\circ \text{ A}$$

Since the source voltages in Figure 3 are in a positive sequence, the line currents are also in a positive sequence.

$$\bar{I}_b = \bar{I}_a\angle -120^\circ = 6.81\angle -141.8^\circ \text{ A}$$

$$\bar{I}_c = \bar{I}_a\angle -240^\circ = 6.81\angle -261.8^\circ = 6.81\angle 98.2^\circ \text{ A}$$

4. A balanced abc -sequence Y -connected source with $\bar{V}_{an} = 100/\underline{10^\circ}$ V is connected to a Δ -connected balanced load $(8 + j4) \Omega$ per phase as shown in Figure 5. Calculate the phase and line currents.

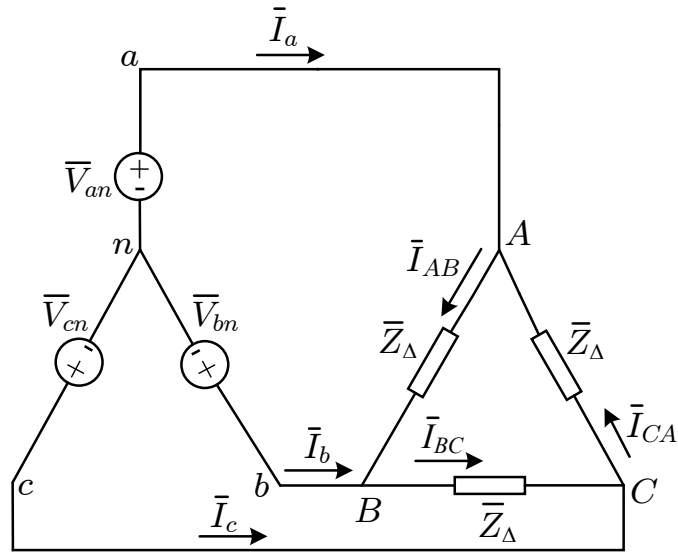


Figure 5 Three-wire $Y - \Delta$ system.

Solution

METHOD 1:

The load impedance is

$$\bar{Z}_{\Delta} = 8 + j4 = 8.944/\underline{26.57^\circ} \Omega$$

The phase voltage $\bar{V}_{an} = 100/\underline{10^\circ}$, then the line voltage is

$$\bar{V}_{ab} = \sqrt{3}\bar{V}_{an}/\underline{30^\circ} = 100\sqrt{3}/\underline{10^\circ + 30^\circ} = \bar{V}_{AB}$$

or,

$$\bar{V}_{AB} = 173.2/\underline{40^\circ}$$

The phase currents are

$$\bar{I}_{AB} = \frac{\bar{V}_{AB}}{\bar{Z}_{\Delta}} = \frac{173.2/\underline{40^\circ}}{8.944/\underline{26.57^\circ}} = 19.36/\underline{13.43^\circ} \text{ A}$$

$$\bar{I}_{BC} = \bar{I}_{AB}/\underline{-120^\circ} = 19.36/\underline{-106.57^\circ} \text{ A}$$

$$\bar{I}_{CA} = \bar{I}_{AB}/\underline{+120^\circ} = 19.36/\underline{133.43^\circ} \text{ A}$$

The line currents are

$$\bar{I}_a = \sqrt{3}\bar{I}_{AB}/\underline{-30^\circ} = \sqrt{3}(19.36)/\underline{13.43^\circ - 30^\circ} = 33.53/\underline{-16.57^\circ} \text{ A}$$

$$\bar{I}_b = \bar{I}_a/\underline{-120^\circ} = 33.53/\underline{-136.57^\circ} \text{ A}$$

$$\bar{I}_c = \bar{I}_a/\underline{+120^\circ} = 33.53/\underline{103.43^\circ} \text{ A}$$

METHOD 2:

Alternatively, using single-phase analysis,

$$\bar{I}_a = \frac{\bar{V}_{an}}{\frac{\bar{Z}_{\Delta}}{3}} = \frac{100/\underline{10^\circ}}{2.981/\underline{26.57^\circ}} = 33.54/\underline{-16.57^\circ} \text{ A}$$

Other line currents are obtained using the abc phase sequence as above.

5. A balanced three-phase system with a line voltage of 300 V supplies a balanced Y-connected load with 1200 W at a leading PF of 0.8. Find the line current and the per-phase load impedance. Further, a balanced 600 W lighting load is added (in parallel) to the system below. Determine the new line current.

Solution

Part A:

The phase voltage is $\frac{300}{\sqrt{3}}$ V and the per-phase power is $\frac{1200}{3} = 400$ W. Thus, the line current may be found from the power relationship.

$$400 = \frac{300}{\sqrt{3}}(|\bar{I}_L|)(0.8)$$

The line current is, therefore, 2.89 A. The phase impedance magnitude is given by

$$|\bar{Z}_p| = \frac{|V_p|}{|I_L|} = \frac{\frac{300}{\sqrt{3}}}{2.89} = 60 \Omega$$

Since the PF is 0.8 leading, the impedance phase angle is $\angle -36.9^\circ$. So, $\bar{Z}_p = 60\angle -36.9^\circ \Omega$.

Part B:

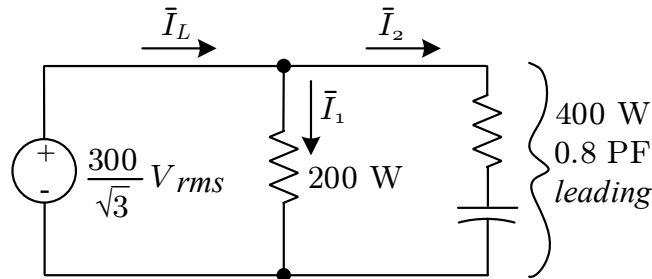


Figure 6 The per-phase equivalent circuit.

The amplitude of the lighting current (labeled $\bar{I}_1$) is determined by

$$200 = \frac{300}{\sqrt{3}}|\bar{I}_1|\cos 0^\circ$$

or,

$$|\bar{I}_1| = 1.155 \text{ A}$$

In a similar way, the amplitude of the capacitive load current (labeled $\bar{I}_2$) is found to be unchanged from its previous value since the voltage across it has remained the same.

$$|\bar{I}_2| = 2.89 \text{ A}$$

If we assume that the phase with which we are working has a phase voltage with an angle of 0° , then since $\cos^{-1}(0.8) = \angle 36.9^\circ$,

$$\bar{I}_1 = 1.155\angle 0^\circ \text{ A}$$

$$\bar{I}_2 = 2.89\angle +36.9^\circ \text{ A}$$

and the line current is

$$\bar{I}_L = \bar{I}_1 + \bar{I}_2 = 3.87\angle +26.6^\circ \text{ A}$$

That's it.